

Computer Architecture (Integer Arithmetic)



विद्याधनं सर्वधनं प्रधानम्

Subhasis Bhattacharjee

Department of Computer Science and Engineering,
Indian Institute of Technology, Jammu


September 18, 2023

Outline I

- ➊ Addition - Single Bit Adder
- ➋ Addition - Multi-Bit Adder
- ➌ Ripple Carry Adder
- ➍ Carry Select Adder
- ➎ Carry Lookahead Adder
- ➏ Integer Multiplication
- ➐ Booth Multiplier
- ➑ Better Way of Adding Partial Products
- ➒ Integer Division
- ➓ Restoring-based Division
- ➔ Non-Restoring-based Division

Addition - Single Bit Adder

Addition - Sum and Carry

 

Truth Table			
Inputs		Outputs	
a	b	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1



Boolean Expressions

$$\text{Sum} = a \oplus b = \bar{a}.b + a.\bar{b}$$

$$\text{Carry} = a.b$$

Symbol	Meaning
.	AND operation
+	OR operation
\oplus	XOR operation

Half Adder

  

Half-Adder adds two 1 bit numbers (say, a and b) to produce 2 bits result (Sum and Carry).

Full Adder

Truth Table				
Inputs			Outputs	
a	b	c_{in}	Sum	c_{out}
0	0	0	0	0
0	1	0	1	0
1	0	0	1	0
1	1	0	0	1
0	0	1	1	0
0	1	1	0	1
1	0	1	0	1
1	1	1	1	1



- It can add three 1 bit numbers (say, a, b, c) to produce a 2 bits (Sum and Carry) output.
- Usually, we take the Carry of previous (lower) bit as the 3rd input in Full-Adder. We call it c_{in} or Carry-In.
- Full Adder produces 2 outputs (Sum and c_{out}).
- c_{out} is termed as Carry out of this addition.

Full Adder - Boolean Expressions

Boolean Expressions for Full Adder

$$\begin{aligned} Sum &= a \oplus b \oplus c_{in} \\ &= a.\overline{b}.\overline{c_{in}} + \overline{a}.b.\overline{c_{in}} + \overline{a}.\overline{b}.c_{in} + a.b.c_{in} \\ c_{out} &= a.b + a.c_{in} + b.c_{in} \end{aligned}$$

Circuit for the Full Adder

  

Addition - Multi-Bit Adder

Addition of two n bit numbers

$$\begin{array}{r} \begin{array}{cccc} \boxed{1} & \boxed{1} & \boxed{1} & \boxed{1} \\ \downarrow & \downarrow & \downarrow & \downarrow \end{array} \\ + \quad 1011 \\ \quad 0101 \\ \hline 10000 \end{array}$$


- We start from the lsb
- Add the corresponding pair of bits and the carry in
- Produce a sum bit and a carry out

Observations - Multi-bit Adder Circuit & Carry Propagation

- We keep adding pairs of bits, and proceed from the lsb to the msb
- If a carry is generated, we add it to the next pair of bits
- At the last step, if a carry is generated, then it becomes the msb of the result
- The carry effectively ripples through the bits

Ripple Carry Adder

Ripple Carry Adder

 

Working of Ripple Carry Adder

A and B are two n-bit Numbers

- Number the bits: A_0 to A_{n-1} and B_0 to B_{n-1}
- lsb $\rightarrow A_0$ and B_0
- msb $\rightarrow A_{n-1}$ and B_{n-1}

Add $A + B$

- Use a half adder to add A_0 and B_0 .
- Send the c_{out} to a full adder that adds: $A_1 + B_1 + c_{in}$.
- Proceed in a similar manner till the msb

Ripple Carry Adder - Computation Time

Time Computation based on Electronic Design / Chip Fabrication Process

- Assume:
 - ▶ Time of half adder: t_h
 - ▶ Time of full adder: t_f
- Total Time Needed for Result: $t_h + (n - 1)t_f$

Time complexity - Let n is the number of bits

Time complexity of a ripple carry adder: $O(n)$

Issues with Ripple Carry Adder - Computation Time

Issues:


- Addition proceeds from lsb to msb - and one bit position at a time.
- It is very slow.
- $O(n)$ is too big for doing just addition of two n -bit numbers.
- How many additions are there in Multiplication of two n -bit numbers.
- Can we find a better Adder?

Carry Select Adder

Carry Select Adder

- Group bits into **Groups** of size (k) bits
- Ex: Adding two 32 bit numbers A and B, and $k = 4$, then we have 8 blocks of 4 bits each.
- Produce the result of each group with a small ripple carry adder.
- In this case, the carry propagates across groups
 - ▶ Time complexity is $O(n)$
 - ▶ Apparently, No benefit.
- But - If all groups compute in parallel / simultaneously
 - ▶ How will a group know the carry of the preceding group?

 Carry Select Adder - Example: 32 bits numbers and $k = 4$



Carry Select Adder - Better Implementation

Stage I: Add the numbers in all Groups in parallel

For each group, produce two results:

- $\{Sum_{Gi}^0, Carry_{Gi}^0\}$ = Assuming an input carry of **0** from previous group.
- $\{Sum_{Gi}^1, Carry_{Gi}^1\}$ = Assuming an input carry of **1** from previous group.

So, for each group we have two results (k-bits sum, 1-bit carry out).

Stage II: Carry Propagation & Finalizing Result


- Start at the least significant block (Input carry is 0).
- Choose the appropriate result from stage I ($\{Sum_{G0}^0, Carry_{G0}^0\}$)
- We now know the input carry $Carry_{G0}^0$ for the second block & Choose the appropriate result
- Result contains the input carry for the third block, and so on \dots .

Carry Select Adder – Stage II - Carry Propagation - Explanation

Stage II: Clarification

- Select the correct carry out of previous group, and,
 - ▶ use this to **select the result** of next group.
 - ▶ How to do this selection?
- This continue until all groups are processed from least-significant group to most-significant group.
- Input carry for least-significant group is 0 (known prior).

Carry Select Adder - Stage I & II

 

Carry Select Adder - Time Requirement

- Stage I:
 - ▶ Each group size is k .
 - ▶ A group takes k units of time (A group is just a Ripple Carry Adder).
- Stage II:
 - ▶ There are n/k groups [i.e., G_0 to $G_{(k-1)}$]
 - ▶ Stage II takes (n/k) units of time (Carry propagation from least-significant group to most-significant group)
 - ▶ Total time : $(k + n/k)$.
- Optimal value of $k = \sqrt{n}$.

Proof: Optimal value of $k = \sqrt{n}$

Total Time (T) = $(k + n/k)$.

We see that, T is **minimized** when $k = n/k$, or, $k^2 = n$, or, $k = \sqrt{n}$.

- What does it signify?
- If $n = 64$ bits, then we should use 8 groups of 8-bits each. And the delay will be 16 units.

Carry Select Adder - Time Complexity

- $T = O(\sqrt{n} + \sqrt{n}) = O(\sqrt{n})$.
- Can we do better?

Carry Lookahead Adder

Carry Lookahead Adder

- The main problem in addition is the carry
- If we have a mechanism to compute the carry quickly, we are done
- Let us thus focus on computing the carry without actually performing an addition

Generate and Propagate Functions

Let us consider two corresponding bits of A and B (A_i and B_i).

Generate function:

- **Generate function:** A new carry is generated. denote as g_i
- $g_i = A_i \cdot B_i$.
- Carry will be generated only if both bits (A_i and B_i) are 1.

Propagate function:

- Whether the bits (A_i and B_i) will propagate the input carry to the next stage? (i.e., Carry-out = carry-in).
- $p_i = A_i \oplus B_i$.
- Carry will be propagated to the next stage if exactly one of the bits (either A_i or B_i) is 1.

g_i and p_i are Generate and Propagate functions at bit level.

Using the g_i & p_i Functions

- If we have the generate and propagate values for a bit pair, we can determine the carry out
- $C_{out} = g_i + p_i \cdot C_{in}$

Example 1: Compute g_i , p_i , and C_{out} .

Given: Let $A_i = 0$, $B_i = 1$. Let the input carry be C_{in} .

Answer:

- $g_i = A_i \cdot B_i = 0 \cdot 1 = 0$
- $p_i = A_i \oplus B_i = 0 \oplus 1 = 1$
- $C_{out} = g_i + p_i \cdot C_{in} = 0 + 1 \cdot C_{in} = C_{in}$

Using the g_i & p_i Functions - Example 2 & 3

Example 2: Compute g_i , p_i , and C_{out} .

Given: Let $A_i = 1$, $B_i = 1$. Let the input carry be C_{in} .

Answer:

- $g_i = A_i \cdot B_i = 1 \cdot 1 = 1$ [i.e., this bit will generate Carry = 1 irrespective of C_{in}].
- $p_i = A_i \oplus B_i = 1 \oplus 1 = 0$
- $C_{out} = g_i + p_i \cdot C_{in} = 1 + 1 \cdot C_{in} = 1$

Example 3: Compute g_i , p_i , and C_{out} .

Given: Let $A_i = 0$, $B_i = 0$. Let the input carry be C_{in} .

Answer:

- $g_i = A_i \cdot B_i = 0 \cdot 0 = 0$
- $p_i = A_i \oplus B_i = 0 \oplus 0 = 0$
- $C_{out} = g_i + p_i \cdot C_{in} = 0 + 0 \cdot C_{in} = 0$

Notations - Summary

Let us consider two corresponding bits of A and B (A_i and B_i).

- $C_{out}^i \rightarrow$ output carry for i^{th} bit pair
- $C_{in}^i \rightarrow$ input carry for i^{th} bit pair
- $g_i \rightarrow$ generate value for i^{th} bit pair
- $p_i \rightarrow$ propagate value for i^{th} bit pair.

Derive Some Carry out bits - $C_{out}^1, C_{out}^2, \dots, C_{out}^n$ - Pg1

C_{out}^1

$$C_{out}^1 = g_1 + p_1 \cdot C_{in}^1$$

C_{out}^2

$$\begin{aligned} C_{out}^2 &= g_2 + p_2 \cdot C_{in}^2 = g_2 + p_2 \cdot C_{out}^1 \\ &= g_2 + p_2 \cdot (g_1 + p_1 \cdot C_{in}^1) \\ &= (g_2 + p_2 \cdot g_1) + p_2 \cdot p_1 \cdot C_{in}^1 \end{aligned}$$

C_{out}^3

$$\begin{aligned} C_{out}^3 &= g_3 + p_3 \cdot C_{in}^3 = g_3 + p_3 \cdot C_{out}^2 \\ &= g_3 + p_3 \cdot ((g_2 + p_2 \cdot g_1) + p_2 \cdot p_1 \cdot C_{in}^1) \\ &= (g_3 + p_3 \cdot g_2 + p_3 \cdot p_2 \cdot g_1) + p_3 \cdot p_2 \cdot p_1 \cdot C_{in}^1 \end{aligned}$$

Derive Some Carry out bits - $C_{out}^1, C_{out}^2, \dots, C_{out}^n$ - Pg2


C_{out}^4

$$\begin{aligned}C_{out}^4 &= g_4 + p_4 \cdot C_{in}^4 = g_4 + p_4 \cdot C_{out}^3 \\&= g_4 + p_4 \cdot ((g_3 + p_3 \cdot g_2 + p_3 \cdot p_2 \cdot g_1) + p_3 \cdot p_2 \cdot p_1 \cdot C_{in}^1) \\&= (g_4 + p_4 \cdot g_3 + p_4 \cdot p_3 \cdot g_2 + p_4 \cdot p_3 \cdot p_2 \cdot g_1) \\&\quad + p_4 \cdot p_3 \cdot p_2 \cdot p_1 \cdot C_{in}^1\end{aligned}$$

G and P for Multibit Systems

1 bit	$C_{out}^1 = \underbrace{g_1}_{G_1} + \underbrace{p_1}_{P_1} \cdot C_{in}^1$
2 bit	$C_{out}^2 = \underbrace{g_2 + p_2 \cdot g_1}_{G_2} + \underbrace{p_2 \cdot p_1}_{P_2} \cdot C_{in}^1$
3 bit	$C_{out}^3 = \underbrace{g_3 + p_3 \cdot g_2 + p_3 \cdot p_2 \cdot g_1}_{G_3} + \underbrace{p_3 \cdot p_2 \cdot p_1}_{P_3} \cdot C_{in}^1$
4 bit	$C_{out}^4 = \underbrace{g_4 + p_4 \cdot g_3 + p_4 \cdot p_3 \cdot g_2 + p_4 \cdot p_3 \cdot p_2 \cdot g_1}_{G_4} + \underbrace{p_4 \cdot p_3 \cdot p_2 \cdot p_1}_{P_4} \cdot C_{in}^1$
n bit	$C_{out}^n = G_n + P_n \cdot C_{in}^1$

Computing G and P Quickly

 

- Let us divide a block of n bits into two parts
- Let the carry out and carry in be: C_{out} and C_{in}
- We want to find the relationship between
- $G_{1,n}$, $P_{1,n}$ and $(G_{m+1,n}, G_{1,m}, P_{m+1,n}, P_{1,m})$
 - ▶ $G_{1,n} \rightarrow$ denotes Carry Generate function for bits from 1 to n .
 - ▶ $P_{1,n} \rightarrow$ denotes Carry Propagation function for bits from 1 to n .

Computing G and P Quickly - II

Computing C_{out}

$$\begin{aligned}C_{out} &= G_{m+1,n} + P_{m+1,n} \cdot C_{sub} \\&= G_{m+1,n} + P_{m+1,n} \cdot (G_{1,m} + P_{1,m} \cdot C_{in}) \\&= [G_{m+1,n} + P_{m+1,n} \cdot G_{1,m}] + [P_{m+1,n} \cdot P_{1,m} \cdot C_{in}] \\&= G_{1,n} + P_{1,n} \cdot C_{in}\end{aligned}$$

Computing G and P

$$\begin{aligned}G_{1,n} &= G_{m+1,n} + P_{m+1,n} \cdot (G_{1,m} \\P_{1,n} &= P_{m+1,n} \cdot P_{1,m}\end{aligned}$$

Insight into Computing G and P quickly

Insight:

- We can compute G and P for a large block
- By first computing G and P for smaller sub-blocks
- And, then combining the solutions to find the value of G and P for the larger block


Fast algorithm to compute G and P:

- Use divide-and-conquer
- Compute G and P functions in $O(\log(n))$ time

Carry Lookahead Adder – Stage I

- Compute G and P functions for all the blocks
- Combine the solutions to find G and P functions for sets of 2 blocks
- Combine the solutions to find G and P functions for sets of 4 blocks
- and, so on...
- Find the G and P functions for a block of size: 32 bits (all bits).


Carry Lookahead Adder – Stage I

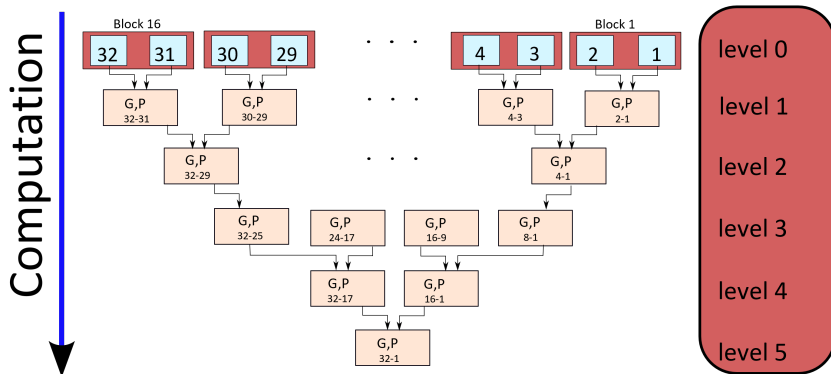

CLA Adder – Stage I

- Compute G, P for increasing sizes of blocks in a tree like fashion
- Time taken :
 - ▶ Total: $\log(n)$ levels
 - ▶ Time per level : $O(1)$
 - ▶ Total Time : $O(\log(n))$

CLA Adder – Stage II

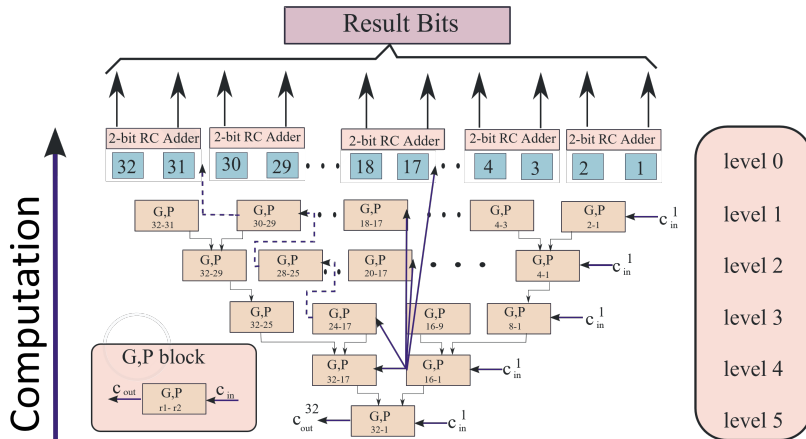

Connection of the G,P Blocks

- Each G,P block represents a range of bits (r_2, r_1) for $(r_2 > r_1)$
 - ▶ The (r_2, r_1) G,P block is connected to all the blocks of the form (r_3, r_2+1)
 - ▶ The carry out of one block is an input to all the blocks that it is connected with
- Each block is connected to another block at the same level, and to blocks at lower levels

Operation of CLA – Stage II

- We start at the leftmost blocks in each level
 - ▶ We feed an input carry value of C_{in1}
 - ▶ Each such block computes the output carry, and sends it to all the blocks that it is connected to
- Each connected block
 - ▶ Computes the output carry
 - ▶ Sends it to all the blocks that it is connected to
- The carry propagates to all the 2 bit RC adders

CLA - Time Complexity

- In a similar manner, the carry propagates to all the RC adders at the zeroth level
- Each of them compute the correct result
- Time taken by Stage II:
 - ▶ Time taken for a carry to propagate from the (16,1) node to the RC adders
 - ▶ $O(\log(n))$
- Time taken by Stage I: $O(\log(n))$
- Total time : $O(\log(n) + \log(n)) = O(\log(n))$

Time Complexities of Various Adders

- Ripple Carry Adder: $O(n)$
- Carry Select Adder: $O(\sqrt{n})$
- Carry Lookahead Adder: $O(\log(n))$

Integer Multiplication

Multiplication Example

$$\begin{array}{r} 13 \\ \times 9 \\ \hline 117 \end{array}$$

$$\begin{array}{r} 1101 \\ \times 1001 \\ \hline 1101 \\ 0000 \\ 0000 \\ 1101 \\ \hline 1110101 \end{array}$$

Partial sums

Multiplicand = 13, Multiplier = 9
Product = 117

Basic Multiplication

- Consider the lsb of the multiplier
 - ▶ If it is 1, write the value of the multiplicand
 - ▶ If it is 0, write 0
- For the next bit of the multiplier
 - ▶ If it is 1, write the value of the multiplicand shifted by 1 position to the left
 - ▶ If it is 0, write 0
- Keep going...

Size of the Product:

If the multiplier has m bits, and the multiplicand has n bits, The product requires $(m+n)$ bits.

Some Definitions

Partial sum:

Partial sum: It is equal to the value of the multiplicand left shifted by a certain number of bits, or it is equal to 0.

Partial product:

Partial product: It is the sum of a set of partial sums.

Multiplying 32 bit numbers

- Let us design an iterative multiplier that multiplies two 32 bit signed values to produce a 64 bit result
- Multiplying two signed 32 bit numbers, and saving the result as a 32 bit number is the same as
- Multiplying two unsigned 32 bit numbers (assuming no overflows)

Theorem on 2's Complement Number

Theorem


A signed n bit number $A = A_{1...n-1} - A_n 2^{n-1}$.

Where,

A_i is the i^{th} bit in A 's 2's complement based binary representation (the first bit i.e., A_1 is the LSB).

$A_{1...n-1}$ is a binary number containing the first $n-1$ digits of A 's binary 2's complement representation.

Iterative Multiplier

 

- Multiplicand (N), Multiplier (M), Product(P) = MN
- U is a 33 bit register and V is a 32 bit register
- beginning: V contains the multiplier, $U = 0$
- UV is one register for the purpose of shifting.

Iterative Multiplication Algorithm

Algorithm 1: Algorithm to multiply two 32 bit numbers and produce a 64 bit result

Data: Multiplier in V , $U = 0$, Multiplicand in N

Result: The lower 64 bits of UV contains the product

```
 $i \leftarrow 0$ 
for  $i < 32$  do
     $i \leftarrow i + 1$ 
    if LSB of  $V$  is 1 then
        if  $i < 32$  then
             $U \leftarrow U + N$ 
        end
        else
             $U \leftarrow U - N$ 
        end
    end
     $UV \leftarrow UV \gg 1$  (arithmetic right shift)
end
```

Example

Multiplicand (N)

0010

2

Multiplier (M)

0011

3

beginning:

U V
00000 0011

1

before shift: 00010 0011

after shift: 00001 0001

2

before shift: 00011 0001

after shift: 00001 1000

3

before shift: 00001 1000

after shift: 00000 1100

4

before shift: 00000 1100

after shift: 00000 0110

Product(P)

0110

6

1 → add 2

1 → add 2

0 → --

0 → --

$$3 * (-2)$$

Multiplicand (N)

0011

3

Multiplier (M)

1110

-2

beginning:

U

V

00000

1110

1

no operation:

00000

1110

after shift:

00000

0111

0



--

2

after add:

00011

0111

after shift:

00001

1011

1



add 3

3

after add:

00100

1011

after shift:

00010

0101

1



add 3

4

after sub:

01111

0101

after shift:

01111

1010

1



sub 3

Product(P)

1010

-6

$$-7 * (-7)$$

Multiplicand (N) 1001 -7

Multiplier (M) 1001 -7

beginning: U V
00000 1001

1 after add: 01001 1001
after shift: 01100 1100

1 → add -7

2 no operation: 01100 1100
after shift: 00110 0110

0 → ----

3 no operation: 00110 0110
after shift: 00011 0011

0 → ----

4 after sub: 01010 0011
after shift: 01100 0001

1 → sub -7

Product(P) -6

11001010

$$-7 * (-7)$$

Multiplicand (N) 1001 -7

Multiplier (M) 1001 -7

beginning: U V
00000 1001

1 after add: 01001 1001
after shift: 00100 1100

1 → add -7

2 no operation: 00100 1100
after shift: 00010 0110

0 → ----

3 no operation: 00010 0110
after shift: 00001 0011

0 → ----

4 after sub: 01000 0011
after shift: 01100 0001

1 → sub -7

Product(P) -6

11001010

Algorithm - Explanation

- Take a look at the lsb of V
 - ▶ If it is 0 \rightarrow do nothing
 - ▶ If it is 1 \rightarrow Add N (multiplicand) to U
- Right shift
 - ▶ Right shifting the partial product is the same as left shifting the multiplicand, which Needs to be done in every step.
- Last step: lsb of V = msb of M (multiplier)
 - ▶ If it is 0 \rightarrow do nothing
 - ▶ If it is 1 then
 - ◆ Multiplier is negative
 - ◆ Recall: $A = A_1 \dots A_{n-1} - A_n 2^{n-1}$.
 - ◆ Hence, we need to subtract the multiplicand if the msb of the multiplier is 1.

Iterative Multiplication - Time Complexity

- There are n loops
 - ▶ Each loop takes $\log(n)$ time
 - ▶ Each time we need to addition & Best Addition (eg, Carry Lookahead Adder) takes $O(\log n)$ time.
- Total time: $O(n \log(n))$

Booth Multiplier

Booth Multiplier

- We can make our iterative multiplier faster
- If there are a continuous sequence of 0s in the multiplier → do nothing
- If there is a continuous sequence of 1s
 - ▶ Assume there is a continuous sequence of 1s from i^{th} bit to j^{th} bit
 - ▶ We Need to perform $(j - i + 1)$ additions.
 - ▶ Can we do something smart?

A continuous sequence of 1s from i^{th} bit to j^{th} bit can be written:

$$M = \sum_{k=i}^{k=j} 2^k = 2^{j+1} - 2^i$$

Booth Multiplication Idea

For a Sequence of 1s

- Subtract the multiplicand when we scan **bit i** (count starts from 0)
- Keep shifting the partial product
- Add the multiplicand(N), when we scan bit ($j+1$)
- This process, effectively adds $(2^{j+1} - 2^i) * N$ to the partial product
- Exactly, what we wanted to do.

Operation of the Algorithm

- Consider bit pairs in the multiplier
- (current bit, previous bit)
- Take actions based on the bit pair
- Action table

(current bit, previous bit)	Action
0,0	-
1,0	subtract multiplicand from U
1,1	-
0,1	add multiplicand to U

Booth's Algorithm

Algorithm 2: Booth's Algorithm to multiply two 32 bit numbers to produce a 64 bit result

Data: Multiplier in V , $U = 0$, Multiplicand in N

Result: The lower 64 bits of UV contain the result

```
 $i \leftarrow 0$   
 $prevBit \leftarrow 0$   
for  $i < 32$  do  
     $i \leftarrow i + 1$   
     $currBit \leftarrow \text{LSB of } V$   
    if  $(currBit, prevBit) = (1, 0)$  then  
         $U \leftarrow U - N$   
    end  
    else if  $(currBit, prevBit) = (0, 1)$  then  
         $U \leftarrow U + N$   
    end  
     $prevBit \leftarrow currBit$   
     $UV \leftarrow UV \gg 1$  (arithmetic right shift)  
end
```

Example 1

Multiplicand (N) 00011 3

Multiplier (M) 0010 2

beginning: U V
00000 0010

1 before shift: 00000 0010
after shift: 00000 0001

2 before shift: 11101 0001
after shift: 11110 1000

3 before shift: 00001 1000
after shift: 00000 1100

4 before shift: 00000 1100
after shift: 00000 0110

Product(P) 0110 6


00 → --

10 → add -3

01 → add 3

00 → --

Example 2

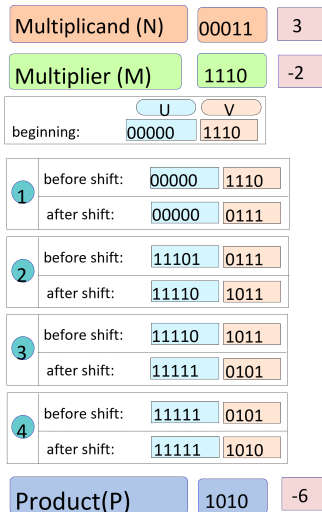

00 → --

10 → add -3

11 → --

11 → --


Booth Algorithm - Time Complexity

- $O(n \log(n))$
- Worst case input (sequence of alternating 0's and 1's)
- Multiplier = 10101010...

Parallel Multiplier

$$\begin{array}{r} \times \quad 1001 \\ \quad 1101 \\ \hline \quad 1001 \\ \quad 0000 \\ \quad 100100 \\ \quad 1001000 \\ \hline \end{array} \quad \left. \vphantom{\begin{array}{r} 1001 \\ 0000 \\ 100100 \\ 1001000 \end{array}} \right\} \text{partial sums}$$

Tree Based Adder for Partial Sums

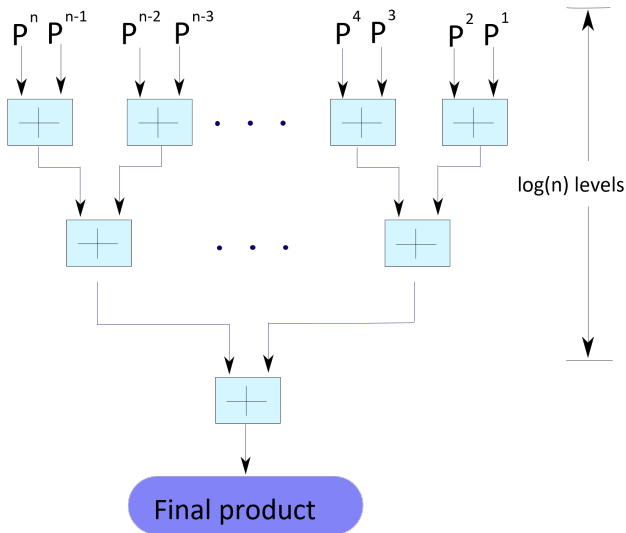


Time Complexity

- There are $\log(n)$ levels
- Each level takes
 - ▶ Maximum $\log(2n)$ time
 - ▶ Adds two $2n$ bit numbers
- Total time: $O(\log(n) * \log(n)) = O(\log(n)^2)$

Better Way of Adding Partial Products

Carry Save Adder

 

- $A + B + C = D + E$
- Takes three numbers, and produces two numbers

Carry Save Adder - Example

Example 1

A	1011
B	1101
C	0001
E	0111
D	1001-

Example 2

A	10111010101011011111000000001101
B	11011110101011011011111011101111
C	00010010101101110101001101010010
E	01110110101101110001110110110000
D	100110101010110111110010010011110

1-bit CSA Adder


- Add three bits - a , b , and c
 - ▶ such that $a + b + c = 2d + e$
 - ▶ d and e are also single bits
- We can conveniently set
 - ▶ e to the sum bit
 - ▶ d to the carry bit⁷⁴

Wallace Tree Multiplier

Basic Idea:

- Generate n partial sums
- Partial sum : $P_i = 0$, if the i^{th} bit in the multiplier is 0
- $P_i = N \ll (i - 1)$, if the the i^{th} bit in the multiplier is 1
- Can be done in parallel: $O(1)$ time
- Add all the n partial sums Use a tree based adder

Tree of CSA Adders

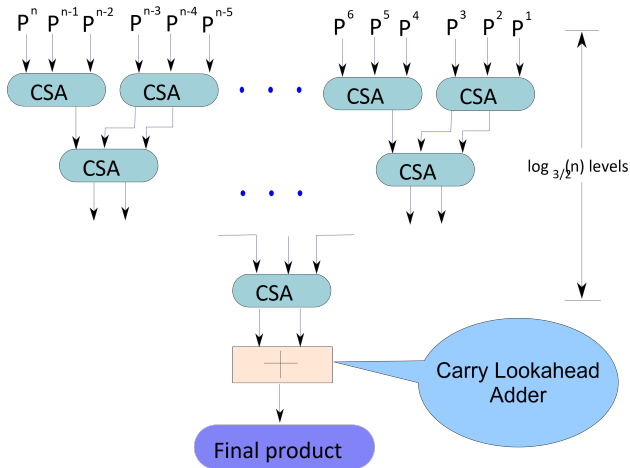

Tree of CSA Adders - Operations

- Group the partial sums into sets of 3
 - ▶ Use an array of CSA adders to add 3 numbers (A,B,C) to produce two numbers (D,E).
 - ▶ Hence, reduce the set of numbers by $2/3$ in each level
- After $\log_{3/2} n$ levels, we are left with only two numbers
 - ▶ size of each number = $2n$ bits.
- Use a CLA adder to add them

Wallace Tree Multiplier - Time Complexity

- Time to generate all the partials sums = $O(1)$
- Time to reduce n partial sums to sum of two numbers
 - ▶ Number of levels $\rightarrow O(\log(n))$
 - ▶ Time per level $\rightarrow O(1)$
 - ▶ Total time for this stage $\rightarrow O(\log(n))$
- Last step
 - ▶ Size of the inputs to the CLA adder $\rightarrow (2n - 1)$ bits
 - ▶ Time taken $\rightarrow O(\log(n))$
- Total Time : $O(\log(n))$

Integer Division


Integer Division

- Let us only consider positive numbers
 - ▶ $N = DQ + R$
 - ▶ $N \rightarrow$ Dividend
 - ▶ $D \rightarrow$ Divisor
 - ▶ $Q \rightarrow$ Quotient
 - ▶ $R \rightarrow$ Remainder
- Properties
 - ▶ Property 1: $R < D, R \geq 0$
 - ▶ Property 2: Q is the largest positive integer satisfying the equation $(N = DQ + R)$ and Property 1

How to Reduce the Problem

- We need to find Q_n
- We can try both values: 0 and 1
 - ▶ First try 1
 - ◆ If: $N - D2^{n-1} \geq 0$, $Q_n = 1$ (maximize the quotient)
 - ▶ Otherwise it is 0
- Once we have reduced the problem
 - ▶ We can proceed recursively

Iterative Divider

 

Initial Value:

V holds the dividend (N), $U = 0$

Restoring-based Division

Restoring Division

Algorithm 3: Restoring algorithm to divide two 32 bit numbers

Data: Divisor in D , Dividend in V , $U = 0$

Result: U contains the remainder (lower 32 bits), and V contains the quotient

```
 $i \leftarrow 0$ 
for  $i < 32$  do
     $i \leftarrow i + 1$ 
    /* Left shift  $UV$  by 1 position */
     $UV \leftarrow UV \ll 1$ 
     $U \leftarrow U - D$ 
    if  $U \geq 0$  then
         $q \leftarrow 1$ 
    end
    else
         $U \leftarrow U + D$ 
         $q \leftarrow 0$ 
    end
    /* Set the quotient bit */
    LSB of  $V \leftarrow q$ 
end
```

Restoring Division - Example

Dividend (N) 00111

Divisor (D) 0011

beginning: U V
00000 0111

1 after shift: 00000 111X
end of iteration: 00000 1110

2 after shift: 00001 110X
end of iteration: 00001 1100

3 after shift: 00011 100X
end of iteration: 00000 1001

4 after shift: 00001 001X
end of iteration: 00001 0010

Quotient(Q) 0010

Remainder(R) 0001

Restoring Division Algorithm - Explanation

Iteratively Do This:

- Consider each bit of the dividend
- Try to subtract the divisor from the U register
 - ▶ If the subtraction is successful, set the relevant quotient bit to 1
 - ▶ Else, set the relevant quotient bit to 0
- Left shift

Restoring Division - Time Complexity

- There are n iterations.
- Each iteration takes $\log(n)$ time
- Total time: $n \log(n)$

Restoring vs Non-Restoring Division

- We need to restore the value of register U
- Requires an extra addition or a register move
- Can we do without this?
 - ▶ Non Restoring Division

Non-Restoring-based Division

Algorithm 4: Non-restoring algorithm to divide two 32 bit numbers

Algorithm 4: Non-restoring algorithm to divide two 32 bit numbers

Data: Divisor in D , Dividend in V , $U = 0$

Result: U contains the remainder (lower 32 bits), and V contains the quotient

```
 $i \leftarrow 0$ 
for  $i < 32$  do
   $i \leftarrow i + 1$ 
  /* Left shift  $UV$  by 1 position */
   $UV \leftarrow UV \ll 1$ 
  if  $U \geq 0$  then
     $U \leftarrow U - D$ 
  end
  else
     $U \leftarrow U + D$ 
  end
  if  $U \geq 0$  then
     $q \leftarrow 1$ 
  end
  else
     $q \leftarrow 0$ 
  end
  /* Set the quotient bit */
  lsb of  $V \leftarrow q$ 
end
if  $U < 0$  then
   $U \leftarrow U + D$ 
end
```

Non-Restoring Division - Example

Dividend (N) 00111

Divisor (D) 0011

beginning:

U	V
00000	0111

1

after shift:	00000	111X
end of iteration:	00000	1110

2

after shift:	00001	110X
end of iteration:	00001	1100

3

after shift:	00011	100X
end of iteration:	00000	1001

4

after shift:	00001	001X
end of iteration:	00001	0010

Quotient(Q) 0010

Remainder(R) 0001