 


Sequential Logic

Subhasis Bhattacharjee

Sequential Networks



Memory: Flip flops

Specification: Finite State Machines


Implementation: Excitation Tables

Memory Devices

- Memory Storage
- Latches
- Flip-Flops
 - SR, D, T

SR (Set/Reset) Latch


- SR Latch

 


- Consider the four possible cases:
 - $S = 1, R = 0$
 - $S = 0, R = 1$
 - $S = 0, R = 0$
 - $S = 1, R = 1$

SR Latch Analysis

 – $S = 1, R = 0$: then $Q = 1$ and $\overline{Q} = 0$




 – $S = 0, R = 1$: then $Q = 0$ and $\overline{Q} = 1$




SR Latch Analysis

 – $S = 1, R = 0$: then $Q = 1$ and $\overline{Q} = 0$



 
– $S = 0, R = 1$: then $Q = 0$ and $\overline{Q} = 1$




SR Latch Analysis

- $S = 0, R = 0$: then $Q = Q_{prev}$


$Q_{prev} = 0$

 


$Q_{prev} = 1$

 

 - $S = 1, R = 1$: then $Q = 0$ and $\overline{Q} = 0$




 


$$y = (S+Q)'$$


$$Q = (R+y)'$$

SR Latch Analysis

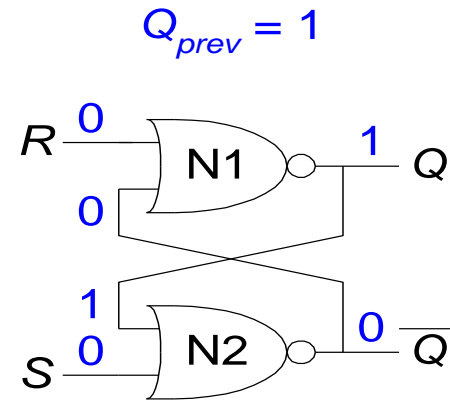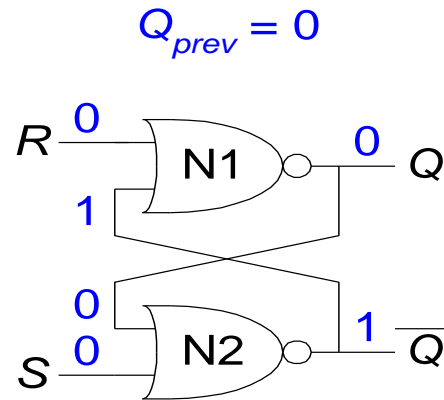- $S = 0, R = 0$: then $Q = Q_{prev}$ and $\bar{Q} = \overline{Q_{prev}}$
(memory!)



 - $S = 1, R = 1$: then $Q = 0$ and $\bar{Q} = 0$ (invalid state: $Q \neq \text{NOT } \bar{Q}$)




SR Latch Symbol

- SR stands for Set/Reset Latch
 - Stores one bit of state (Q)
- Control what value is being stored with S , R inputs
 - **Set:** Make the output 1 ($S = 1$, $R = 0$, $Q = 1$)
 - **Reset:** Make the output 0 ($S = 0$, $R = 1$, $Q = 0$)

- **Must do something to avoid invalid state (when $S = R = 1$)**


SR Latch
Symbol

 


D Latch

- Two inputs: CLK , D
 - CLK : controls *when* the output changes
 - D (the data input): controls *what* the output changes to
- Function
 - When $CLK = 1$, D passes through to Q (the latch is *transparent*)
 - When $CLK = 0$, Q holds its previous value (the latch is *opaque*)
- Avoids invalid case when $Q \neq \text{NOT } \bar{Q}$

D Latch
Symbol

 


D Latch Internal Circuit

 

CLK	D	\overline{D}	S	R	Q	\overline{Q}
0	X					
1	0					
1	1					

D Latch Internal Circuit

 


CLK	D	\overline{D}	S	R	Q	\overline{Q}
0	X	\overline{X}	0	0	Q_{prev}	\overline{Q}_{prev}
1	0	1	0	1	0	1
1	1	0	1	0	1	0

D Flip-Flop


- Two inputs: CLK , D
- *Function*
 - The flip-flop “samples” D on the rising edge of CLK
 - When CLK rises from 0 to 1, D passes through to Q
 - Otherwise, Q holds its previous value
 - Q changes only on the rising edge of CLK
- A flip-flop is called an *edge-triggered* device because it is activated on the clock edge

D Flip-Flop
Symbols



 


D Flip-Flop Internal Circuit



 
- Two back-to-back latches (L1 and L2) controlled by complementary clocks
- When $CLK = 0$
 - L1 is transparent, L2 is opaque
 - D passes through to N1
- When $CLK = 1$
 - L2 is transparent, L1 is opaque
 - N1 passes through to Q
- Thus, on the edge of the clock (when CLK rises from $0 \rightarrow 1$)
 - D passes through to Q




D Flip-Flop vs. D Latch

   

D Flip-Flop vs. D Latch

   

D Flip-Flop (Delay)

 

Id	D	Q(t)	Q(t+1)
0	0	0	0
1	0	1	0
2	1	0	1
3	1	1	1

State table

PS \ D	0	1
0	0	1
1	0	1

NS = Q(t+1)

Characteristic Expression
 $Q(t+1) = D(t)$



Sequential Modules: Introduction

- Slice operation bitwise
- Perform process in a series of time
- Advantage:
 - Cheaper hardware
 - Fit for FPGA architecture
 - Pipelining for excellent throughput
- Disadvantage: Longer latency


Serial Adder: Perform serial bit-addition

At time i , read a_i and b_i . Produce s_i and c_{i+1}

  Internal state stores c_i . Carry bit c_0 is set as c_{in}



Serial Adder using D F-F

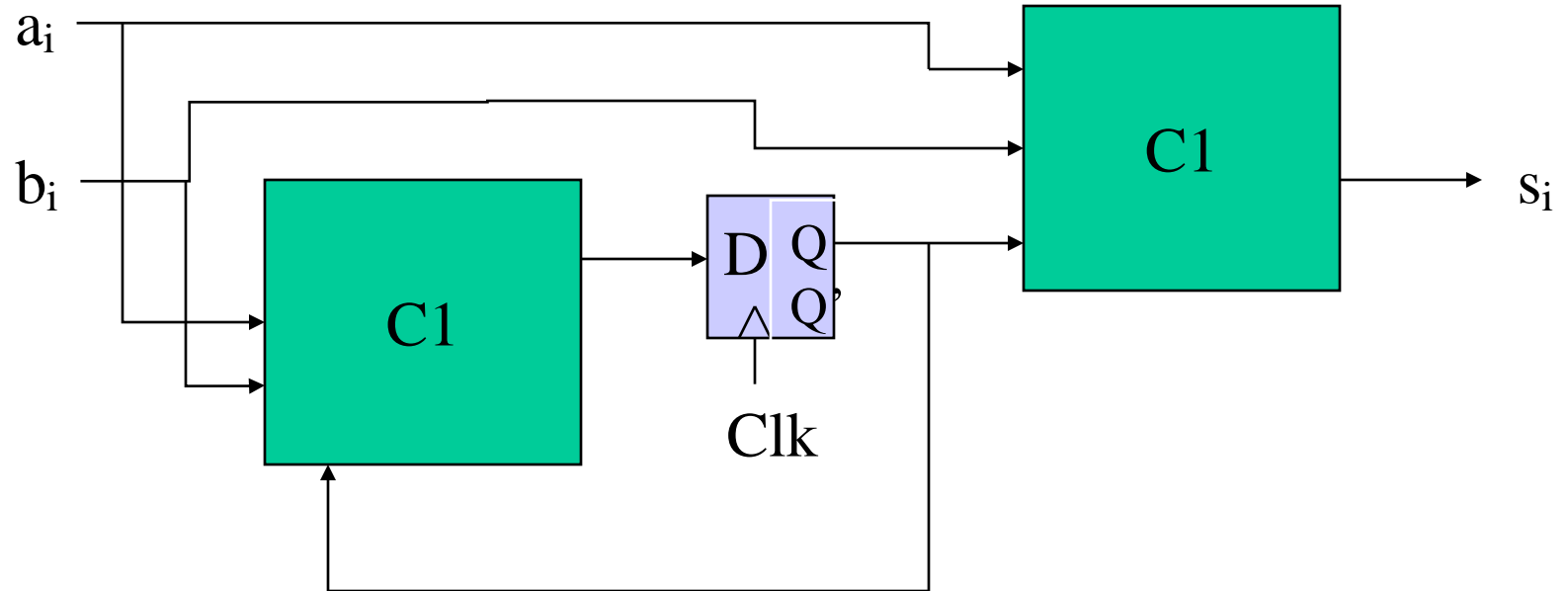

Feed a_i and b_i and generate s_i at time i .
Where is c_i and c_{i+1} ?

Serial Adder using a D Flip-Flop


id	a_i	b_i	c_i	c_{i+1}	s_i
0	0	0	0	0	0
1	0	0	1	0	1
2	0	1	0	0	1
3	0	1	1	1	0
4	1	0	0	0	1
5	1	0	1	1	0
6	1	1	0	1	0
7	1	1	1	1	1

$$D=c_{i+1}$$

$$Q=c_i$$

Serial Adder using a D Flip-Flop

Logic Diagram

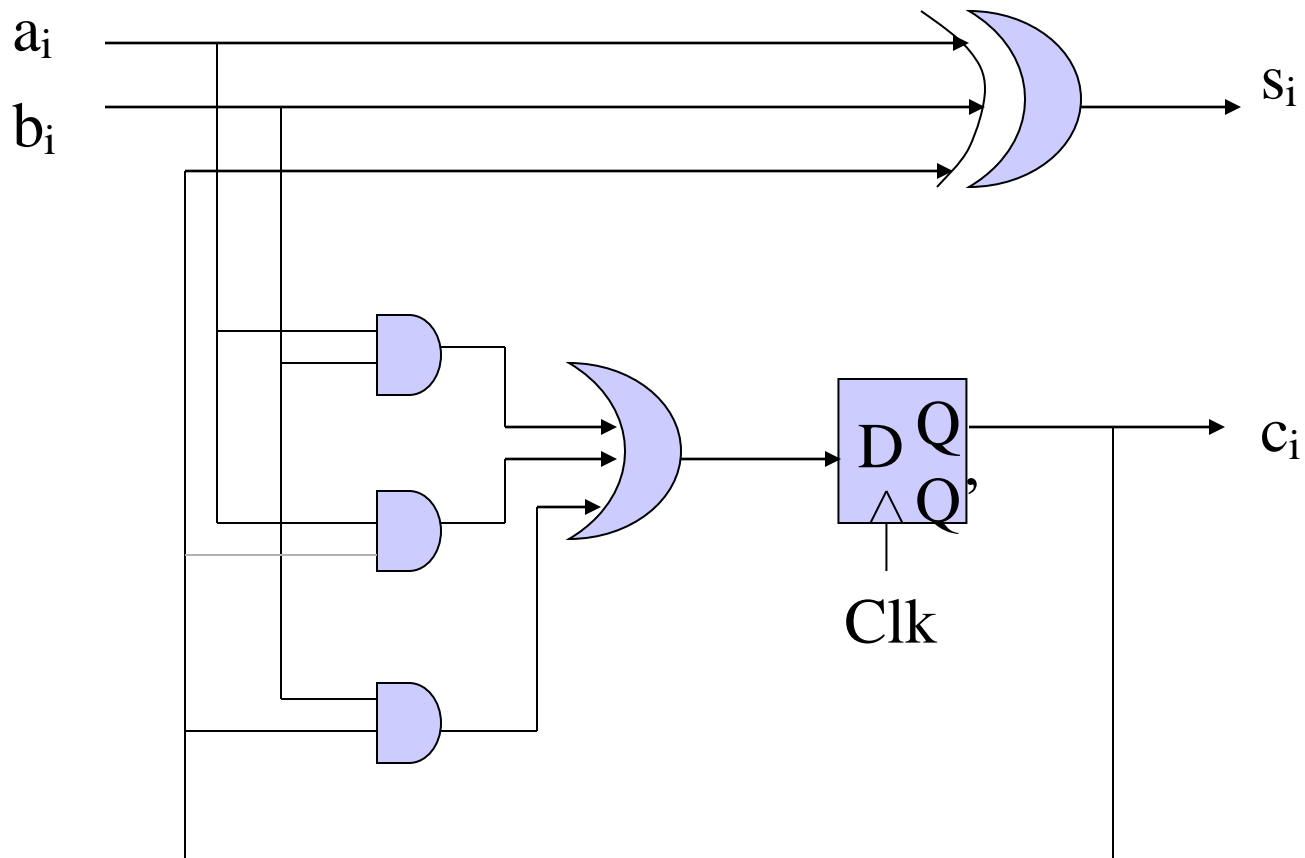

Serial Adder using an SR Flip-Flop

Excitation Table

id	a_i	b_i	c_i (Q)	c_{i+1}	S	R
0	0	0	0	0	0	-
1	0	0	1	0	0	1
2	0	1	0	0	0	-
3	0	1	1	1	-	0
4	1	0	0	0	0	-
5	1	0	1	1	-	0
6	1	1	0	1	1	0
7	1	1	1	1	-	0

SR generate c_{i+1}
 $Q=c_i$

Excitation Table of SR Flip-Flop

S

	b_i			
	0	0	1	0
c_i	0	-	-	-
	a_i			

State table

inputs		SR			
PS		00	01	10	11
0		0	0	1	-
1		1	0	1	-
		Q(t+1)			

R

	b_i			
	-	-	0	-
c_i	1	0	0	0
	a_i			

Excitation table


NS		Q(t+1)	
PS		0	1
Q(t)	0	0 -	1 0
	1	0 1	- 0

Serial Adder using an SR Flip-Flop

Logic Diagram

$$S = a_i b_i$$

$$R = a_i' b_i'$$

 

Multiplication using Serial Addition

$$3 \times 5 = 15$$

$$\begin{array}{r}
 \\
 + \quad 0 \quad 1 \quad 1 \quad 1 \quad 1 \\
 \hline
 \end{array}$$

[illegible]

For $\mathbf{m}=\mathbf{A}\times\mathbf{B}$, set $\mathbf{m}^{(0)}=\mathbf{0}$

At time i , perform $\mathbf{m}^{(i+1)} = \mathbf{m}^{(i)} + \mathbf{A} \mathbf{b}_i 2^i$

Standard Sequential Modules

1. Register
2. Shift Register
3. Counter

Register

We Will Study Rest of the Topics
Later on

Shift Register

Counter


Counter: Applications

- Program Counter
- Address Keeper: FIFO, LIFO
- Clock Divider
- Sequential Machine

Counter

- Modulo-n Counter
- Modulo Counter ($m < n$)
- Counter (a-to-b)
- Counter of an Arbitrary Sequence
- Cascade Counter


Modulo-n Counter

 

$Q(t+1)$	$= (0, 0, \dots, 0)$	if $CLR = 1$
	$= D$	if $LD = 1$ and $CLR = 0$
	$= (Q(t)+1) \bmod n$	if $LD = 0, CNT = 1$ and $CLR = 0$
	$= Q(t)$	if $LD = 0, CNT = 0$ and $CLR = 0$
TC	$= 1$	if $Q(t) = n-1$ and $CNT = 1$
	$= 0$	otherwise

Modulo-m Counter ($m < n$)

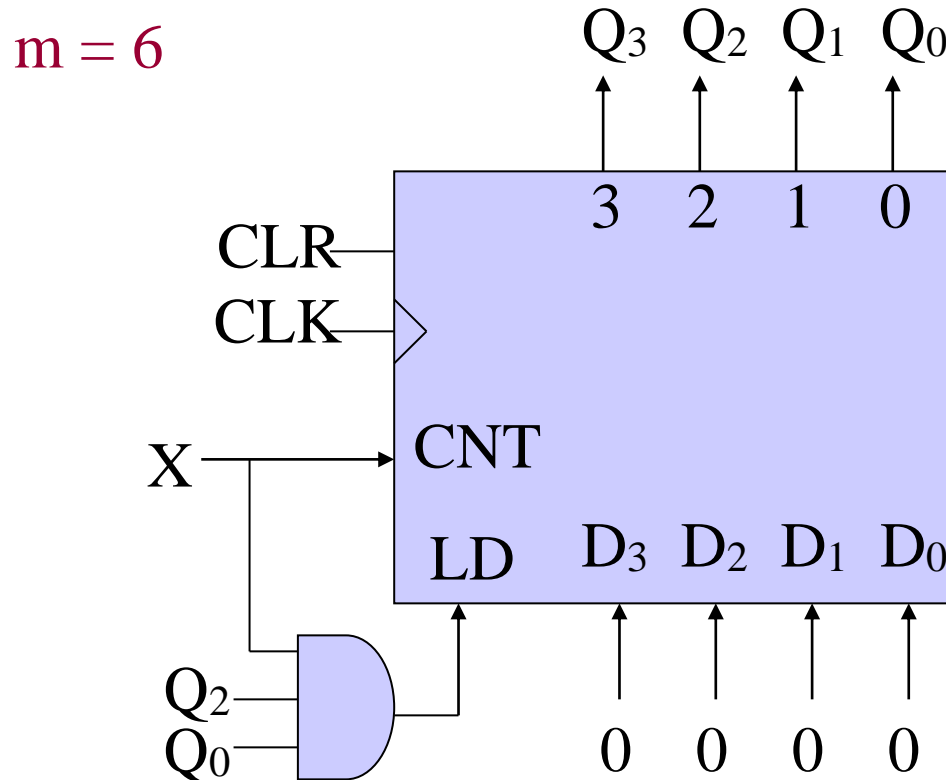Given a mod 16 counter, construct
a mod-m counter ($0 < m < 16$) with AND, OR, NOT gates




Set $LD = 1$ when $X = 1$ and $(Q_3Q_2Q_1Q_0) = (0101)$, ie $m-1$

Counter (a-to-b)

Given a mod 16 counter, construct an a-to-b counter
($0 < a < b < 16$)

A 5-to-11 Counter

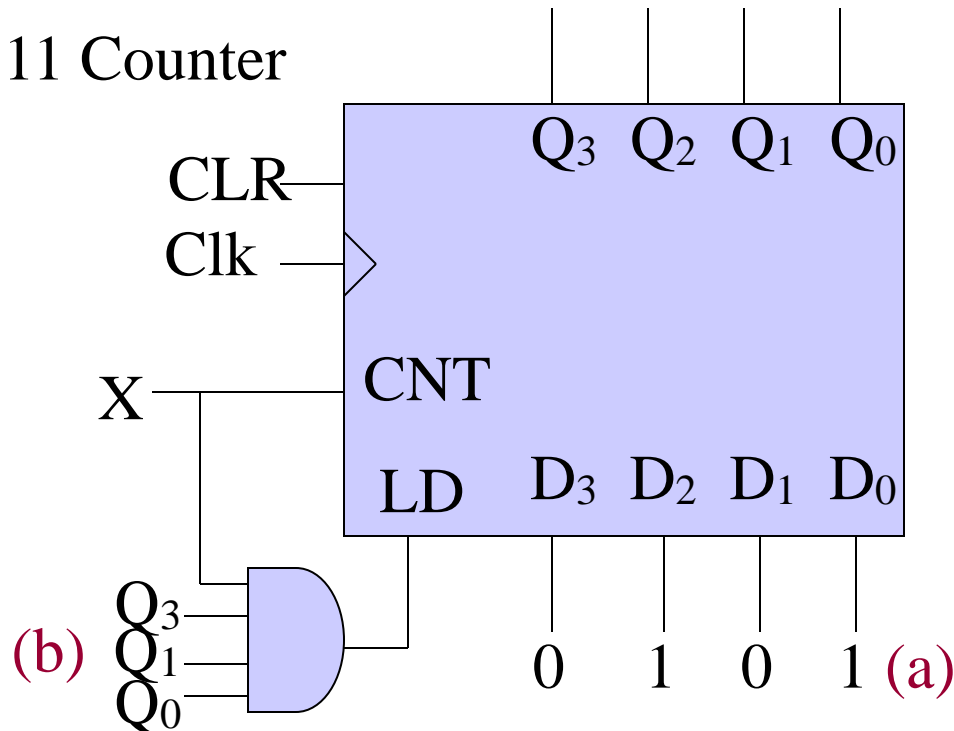

Set LD = 1 when $X = 1$ and $(Q_3Q_2Q_1Q_0) = b$ (in this case, 1011)

Counter of an Arbitrary Sequence

Given a mod 8 counter, construct
a counter with sequence 0 1 5 6 2 3 7

When $Q = 1$, load $D = 5$

When $Q = 6$, load $D = 2$

When $Q = 3$, load $D = 7$

