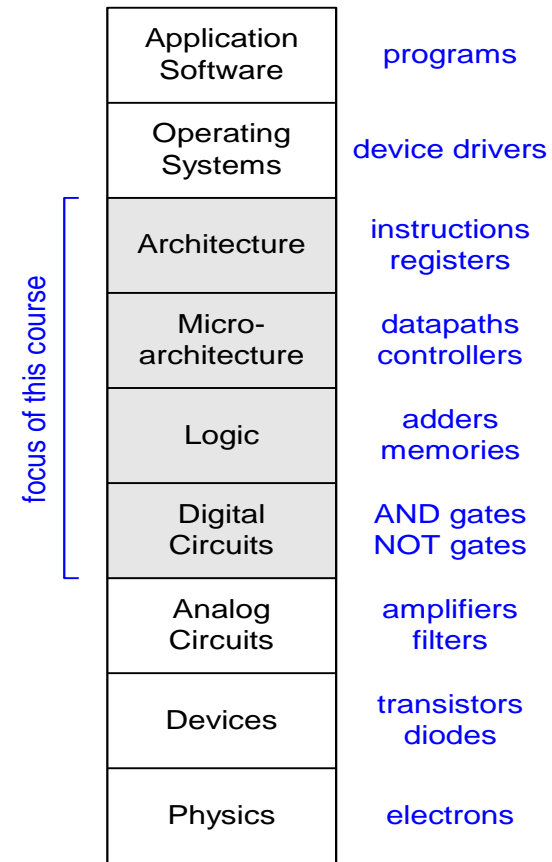


Introduction to Digital Logic Design

Subhasis Bhattacharjee

Scope




Major Parts in this course

We will cover the following major things in this course:


- Combinational Logic
- Sequential Networks
- Standard Modules

 Combinational Logic vs Sequential Network



Combinational logic:

$$y_i = f_i(x_1, \dots, x_n)$$

 

Sequential Networks

1) Memory 2) Time Steps (Clock)

$$y_i^t = f_i(x_1^t, \dots, x_n^t, s_1^t, \dots, s_m^t)$$


$$s_i^{t+1} = g_i(x_1^t, \dots, x_n^t, s_1^t, \dots, s_m^t)$$

Scope

| Subjects | Building Blocks | Theory |
|---------------------|----------------------------------|------------------------------|
| Combinational Logic | AND, OR, NOT,XOR | Boolean Algebra |
| Sequential Network | FF, Counter, Registers | Finite State Machine |
| Standard Modules | Operators, Interconnects, Memory | Arithmetics, Universal Logic |


George Boole, 1815 - 1864

 - Born to working class parents
- Taught himself mathematics and joined the faculty of Queen's College in Ireland.
- Wrote *An Investigation of the Laws of Thought* (1854)
- Introduced binary variables
- Introduced the three fundamental logic operations: AND, OR, and NOT.



Combinational Logic

 Combinational Logic vs Boolean Algebra Expression



Schematic Diagram:

5 primary inputs

4 components

9 signal nets

12 pins

Boolean Algebra:

5 literals

4 operators

Some Definitions

- Complement: variable with a bar over it

$\bar{A}, \bar{B}, \bar{C}$

- Literal: variable or its complement

$A, \bar{A}, B, \bar{B}, C, \bar{C}$

- Implicant: product of literals

$A\bar{B}C, A\bar{C}, BC$

- Minterm: product that includes all input variables

$\bar{A}BC, AB\bar{C}, A\bar{B}C$

- Maxterm: sum that includes all input variables

$(A+\bar{B}+C), (\bar{A}+B+C), (\bar{A}+\bar{B}+\bar{C})$

Digital Discipline: Binary Values

- Typically consider only two discrete values:
 - 1's and 0's
 - 1, TRUE, HIGH
 - 0, FALSE, LOW
- 1 and 0 can be represented by specific voltage levels, rotating gears, fluid levels, etc.
- Digital circuits usually depend on specific voltage levels to represent 1 and 0
- *Bit: Binary digit*

Digital (logic) Elements: Gates

- Digital devices or gates have one or more inputs and produce an output that is a function of the current input value(s).
- All inputs and outputs are binary and can only take the values 0 or 1
- A gate is called a *combinational circuit* because the output only depends on the current input combination.
- Digital circuits are created by using a number of connected gates such as the output of a gate is connected to the input of one or more gates in such a way to achieve specific outputs for input values.
- Digital or logic design is concerned with the design of such circuits.


Truth Tables

Provide a **listing** of every possible combination of values of binary inputs to a digital circuit and the corresponding outputs.


| INPUTS | OUTPUTS |
|--------|---------|
| ... | ... |
| ... | ... |

| Truth Table | | | |
|-------------|---|-------------|---------|
| Inputs | | Outputs | |
| x | y | $x \cdot y$ | $x + y$ |
| 0 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 |
| 1 | 1 | 1 | 1 |

- Example (2 inputs, 2 outputs):

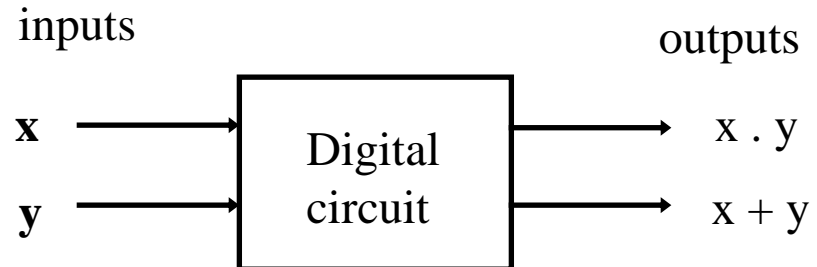


AND Gate

 

| Truth Table | | |
|-------------|---|--------|
| Inputs | | Output |
| A | B | A.B |
| 0 | 0 | 0 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | 1 |

| SHARED TERMINALS (We will not mention them - Usually) | |
|--|--|
| GND | Connected to ground |
| VCC | Connected to positive voltage to provide power to all four gates |


OR Gate

 

Symbol

| Truth Table | | |
|-------------|---|--------|
| Inputs | | Output |
| A | B | A + B |
| 0 | 0 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 1 |

NAND Gate

 


Symbol

| Truth Table | | |
|-------------|---|----------------|
| Inputs | | Output |
| A | B | $(A \cdot B)'$ |
| 0 | 0 | 1 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 0 |

The NAND Gate





 
- Multiple equivalent symbols / logical representations
- NAND gate is self-sufficient (can build any logic circuit with it).
- Can be used to implement AND/OR/NOT








Equivalent Symbols

Logic Gates

Symbol set 1

     

     Symbol set 2
(ANSI/IEEE Standard 91-1984)



Useful Circuits using Logic Gates

Binary Addition

$$\begin{array}{r}
 5 \\
 + 7 \\
 \hline
 \end{array}$$

1 2

 ↗ ←

 Carry Sum


$$\begin{array}{r}
 \begin{array}{cccc}
 & 1 & 1 & 1 & \leftarrow \text{Carry bits} \\
 & & 1 & 0 & 1 \\
 + & & 1 & 1 & 1 \\
 \hline
 \end{array} \\
 \begin{array}{cccc}
 \text{Carryout} & 1 & 1 & 0 & 0 \\
 & \nwarrow & & \nearrow & \\
 & & \text{Sums} & &
 \end{array}
 \end{array}$$

5
7
12

Binary Addition: Hardware

- Half Adder: Two inputs (a,b) and two outputs (carry, sum).
- Full Adder: Three inputs (a,b,c) and two outputs (carry, sum).

Half Adder

 

Truth Table

| a | b | carry | sum |
|---|---|-------|-----|
| 0 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 |
| 1 | 1 | 1 | 0 |

Switching Function

Switching Expressions:

$$\text{Sum (a,b)} = a'b + ab'$$



$$\text{Carry (a, b)} = a*b$$

Ex:

$$\text{Sum (0,0)} = 0'0 + 0*0' = 0 + 0 = 0$$


$$\text{Sum (0,1)} = 0'1 + 0*1' = 1 + 0 = 1$$
  
$$\text{Sum (1,1)} = 1'1 + 1*1' = 0 + 0 = 0$$



Full Adder

Truth Table

 

| Id | a | b | c_{in} | carry | sum |
|----|---|---|----------|-------|-----|
| 0 | 0 | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 1 | 0 | 1 |
| 2 | 0 | 1 | 0 | 0 | 1 |
| 3 | 0 | 1 | 1 | 1 | 0 |
| 4 | 1 | 0 | 0 | 0 | 1 |
| 5 | 1 | 0 | 1 | 1 | 0 |
| 6 | 1 | 1 | 0 | 1 | 0 |
| 7 | 1 | 1 | 1 | 1 | 1 |

Minterm and Maxterm

| Id | a | b | c _{in} | carryout | |
|----|---|---|-----------------|----------|----------|
| 0 | 0 | 0 | 0 | 0 | $a+b+c$ |
| 1 | 0 | 0 | 1 | 0 | $a+b+c'$ |
| 2 | 0 | 1 | 0 | 0 | $a+b'+c$ |
| 3 | 0 | 1 | 1 | 1 | $a' b c$ |
| 4 | 1 | 0 | 0 | 0 | $a'+b+c$ |
| 5 | 1 | 0 | 1 | 1 | $a b' c$ |
| 6 | 1 | 1 | 0 | 1 | $a b c'$ |
| 7 | 1 | 1 | 1 | 1 | $a b c$ |

\uparrow
 minterm

\nwarrow
 maxterm

Minterms

$$f_1(a,b,c) = a'bc + ab'c + abc' + abc$$

$$a'bc = 1 \text{ iff } (a,b,c) = (0,1,1)$$

$$ab'c = 1 \text{ iff } (a,b,c) = (1,0,1)$$

$$abc' = 1 \text{ iff } (a,b,c) = (1,1,0)$$

$$abc = 1 \text{ iff } (a,b,c) = (1,1,1)$$

$$f_1(a,b,c) = 1 \text{ iff } (a,b,c) = (0,1,1), (1,0,1), (1,1,0), \text{ or } (1,1,1)$$

$$\text{Ex: } f_1(1,0,1) = 1'01 + 10'1 + 101' + 101 = 1$$

$$f_1(1,0,0) = 1'00 + 10'0 + 100' + 100 = 0$$

Maxterms

$$f_2(a,b,c) = (a+b+c)(a+b+c')(a+b'+c)(a'+b+c)$$

$$a + b + c = 0 \text{ iff } (a,b,c) = (0,0,0)$$

$$a + b + c' = 0 \text{ iff } (a,b,c) = (0,0,1)$$

$$a + b' + c = 0 \text{ iff } (a,b,c) = (0,1,0)$$

$$a' + b + c = 0 \text{ iff } (a,b,c) = (1,0,0)$$


$$f_2(a,b,c) = 0 \text{ iff } (a,b,c) = (0,0,0), (0,0,1), (0,1,0), (1,0,0)$$

$$\text{Ex: } f_2(1,0,1) = (1+0+1)(1+0+1')(1+0'+1)(1'+0+1) = 1$$

$$f_2(0,1,0) = (0+1+0)(0+1+0')(0+1'+0)(0'+1+0) = 0$$

Other - Two-Input Logic Gates


XOR

 

$$Y = A \oplus B$$

| A | B | Y |
|---|---|---|
| 0 | 0 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 0 |


NAND

 

$$Y = \overline{AB}$$

| A | B | Y |
|---|---|---|
| 0 | 0 | 1 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 0 |


NOR

 

$$Y = \overline{A + B}$$

| A | B | Y |
|---|---|---|
| 0 | 0 | 1 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | 0 |

XNOR

 

$$Y = \overline{A \oplus B}$$

| A | B | Y |
|---|---|---|
| 0 | 0 | 1 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | 1 |

Which Gates are Important

Universal Set

Universal Set: A set of gates such that every switching function can be implemented with gates in this set.

Ex:

{AND, OR, NOT}

{AND, NOT}

{OR, NOT}

Universal Set

Universal Set: A set of gates such that every Boolean function can be implemented with gates in this set.

Ex:

{AND, OR, NOT}

{AND, NOT} OR can be implemented with AND & NOT gates $a+b = (a'b')'$

{OR, NOT} AND can be implemented with OR & NOT gates $ab = (a'+b')'$

{AND, OR} This is not universal.

Standard Combinational Modules (Combinational Building Blocks)

Some (Common) Building Blocks?

- Decoder: Decode address
- Encoder: Encode address
- Multiplexer (Mux): Select data by address
- Demultiplexier (DeMux): Direct data by address
- Shifter: Shift bit location
- Adder: Add two binary numbers

Part III. Standard Modules

Interconnect Modules:


1. Decoder, 2. Encoder

3. Multiplexer, 4. Demultiplexer

Multiplexer


- Definition
- Logic Diagram
- Application

3. Mux (Multiplexer): Definition

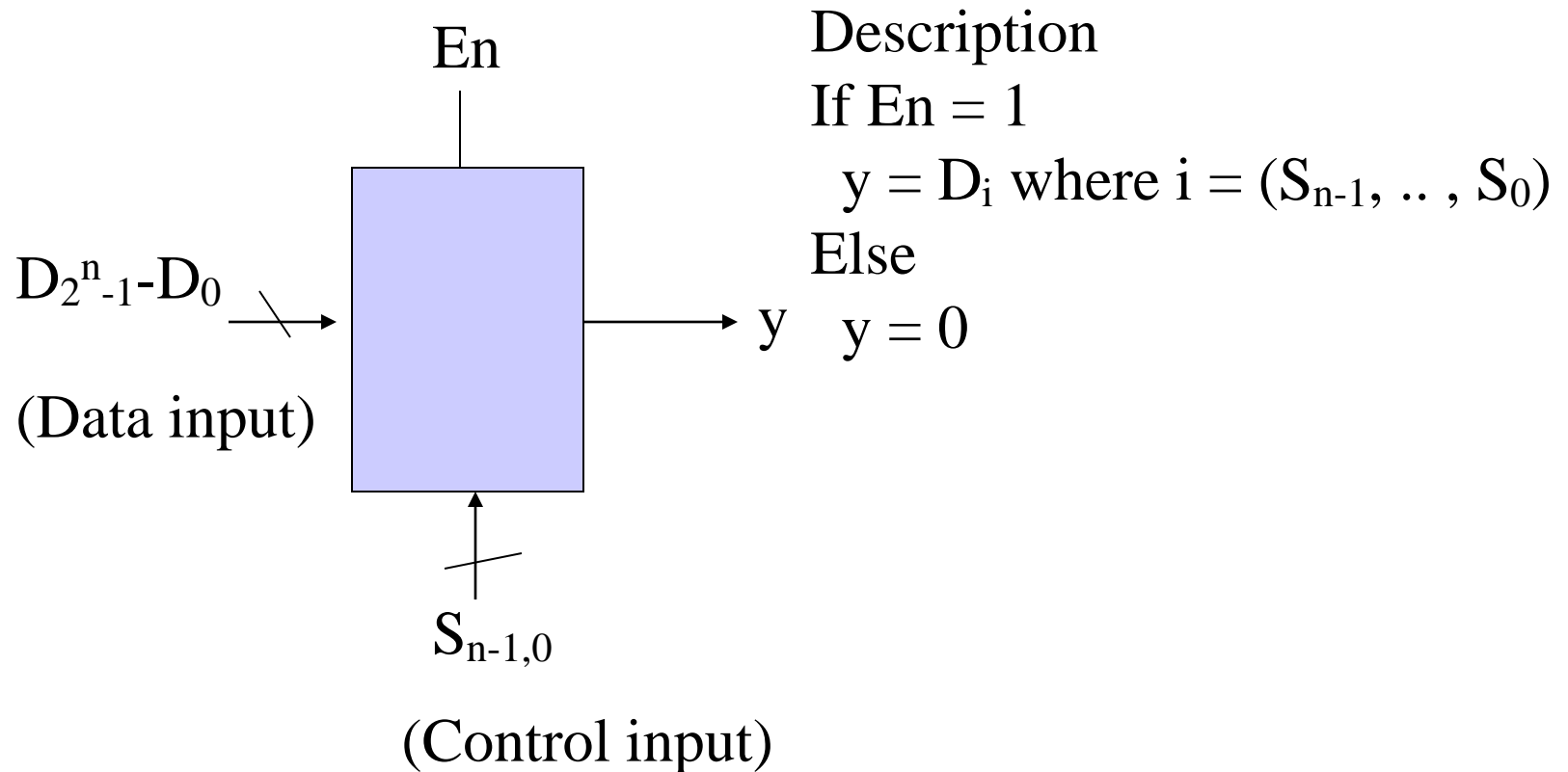

Multiplexer (Mux): Definition

 
- Selects between one of N inputs to connect to the output.
- $\log_2 N$ -bit select input – control input
- Example:



2:1 Mux

| S | D_1 | D_0 | Y | S | Y |
|-----|-------|-------|-----|-----|-------|
| 0 | 0 | 0 | 0 | 0 | D_0 |
| 0 | 0 | 1 | 1 | 1 | D_1 |
| 0 | 1 | 0 | 0 | | |
| 0 | 1 | 1 | 1 | | |
| 1 | 0 | 0 | 0 | | |
| 1 | 0 | 1 | 0 | | |
| 1 | 1 | 0 | 1 | | |
| 1 | 1 | 1 | 1 | | |

Multiplexer Definition: Example

 

If $D_0 = 0$ and $S_1S_0 = 00 \Rightarrow y = 0$


If $D_0 = 1$ and $S_1S_0 = 00 \Rightarrow y = 1$

Multiplexer: Logic Diagram


- Logic gates
 - Sum-of-products form

| Y S | $D_0 D_1$ | | | |
|--------|-----------|----|----|----|
| | 00 | 01 | 11 | 10 |
| 0 | 0 | 0 | 1 | 1 |
| 1 | 0 | 1 | 1 | 0 |


$$Y = D_0 \bar{S} + D_1 S$$

 

 
- Tristates
 - For an N-input mux, use N tristates
 - Turn on exactly one to select the appropriate input



4. Demultiplexers

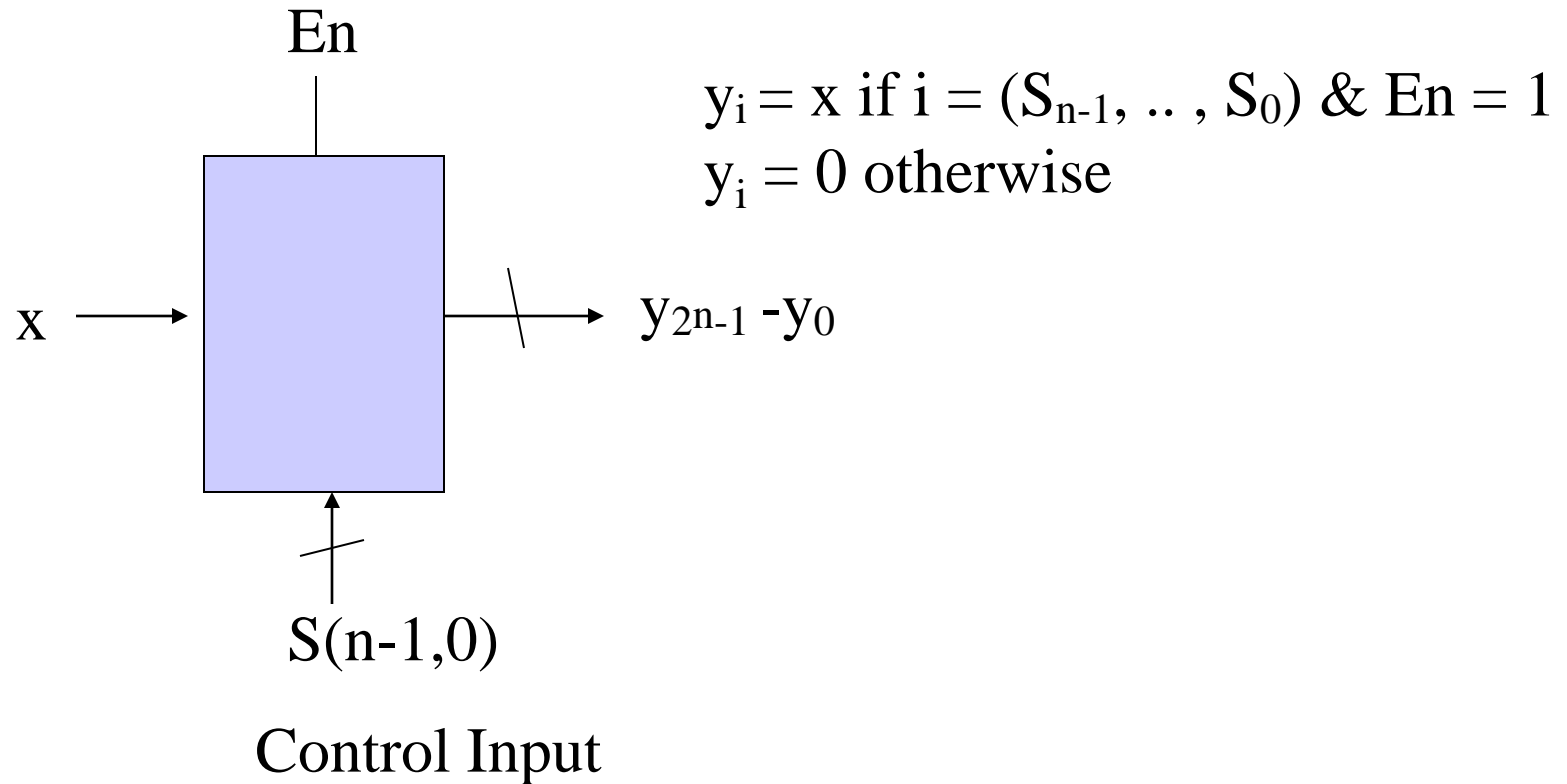


Shifter


 


$$\begin{aligned}
 y_i &= x_{i-1} \text{ if } En = 1, s = 1, \text{ and } d = L \\
 &= x_{i+1} \text{ if } En = 1, s = 1, \text{ and } d = R \\
 &= x_i \text{ if } En = 1, s = 0 \\
 &= 0 \text{ if } En = 0
 \end{aligned}$$


Can be implemented with a mux

 

Barrel Shifter

 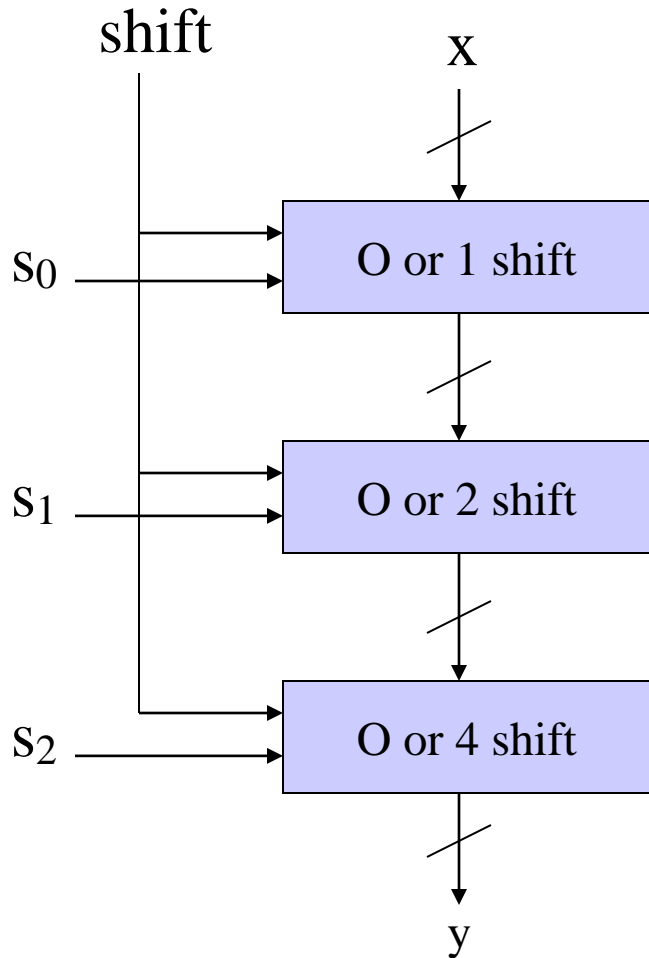

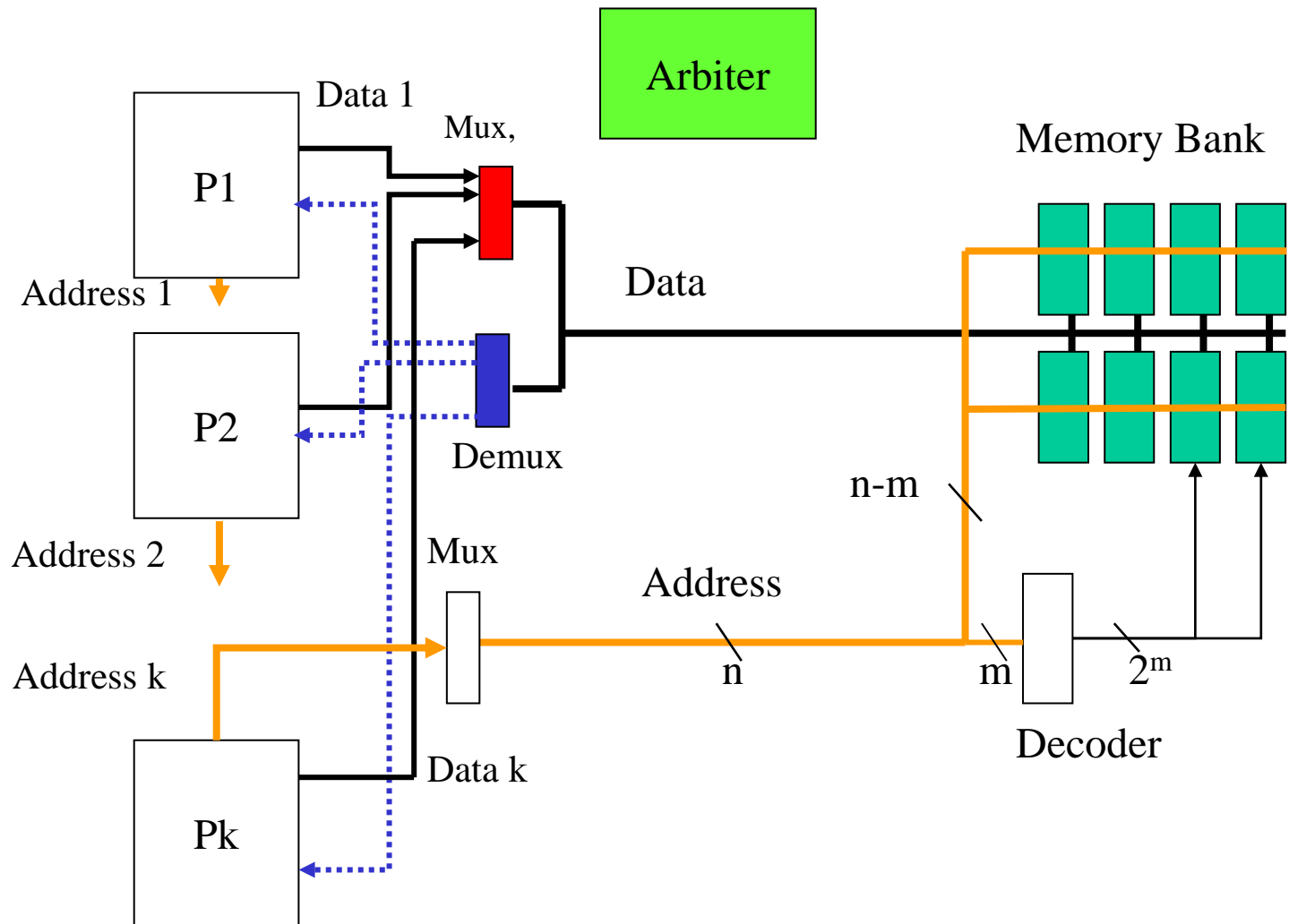
Interconnect: Decoder, Encoder, Mux, DeMux



1. Decoder

- Definition
- Logic Diagram
- Application (Universal Set)
- Tree of Decoders

1. Decoder: Definition

 


n to 2^n decoder
function:

$$y_i = 1 \text{ if } E_n = 1 \text{ \& } (I_2, I_1, I_0) = i$$
$$y_i = 0 \text{ otherwise}$$

 
1. Decoder: Definition

- N inputs, 2^N outputs
- One-hot outputs: only one output HIGH at once



| A_1 | A_0 | Y_3 | Y_2 | Y_1 | Y_0 |
|-------|-------|-------|-------|-------|-------|
| 0 | 0 | 0 | 0 | 0 | 1 |
| 0 | 1 | 0 | 0 | 1 | 0 |
| 1 | 0 | 0 | 1 | 0 | 0 |
| 1 | 1 | 1 | 0 | 0 | 0 |

Decoder: Logic Diagram




 


Decoder Application: universal set {Decoder, OR}

Example: Implement functions $f_1(a,b,c) = \Sigma m(1,2,4)$


$f_2(a,b,c) = \Sigma m(2,3)$, and $f_3(a,b,c) = \Sigma m(0,5,6)$

with a 3-input decoder and OR gates.

    


Decoders

- OR minterms

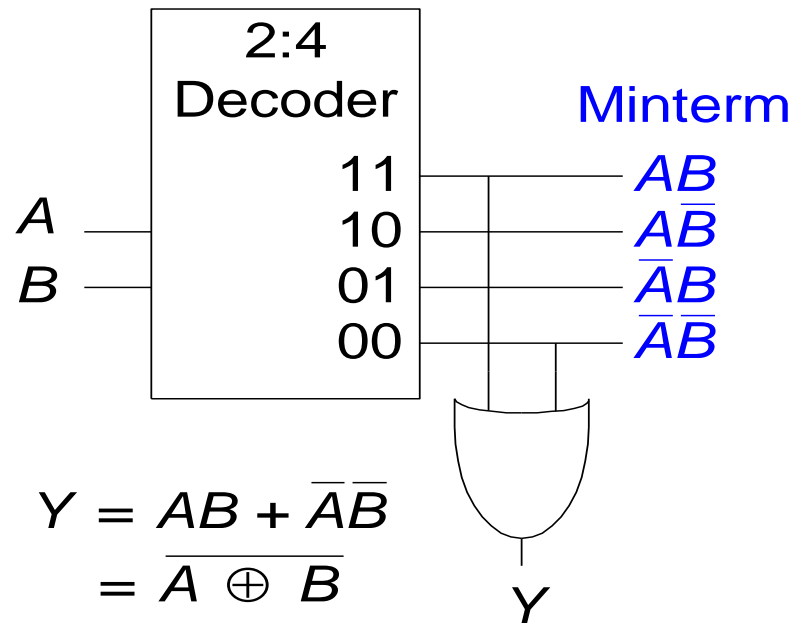


Tree of Decoders

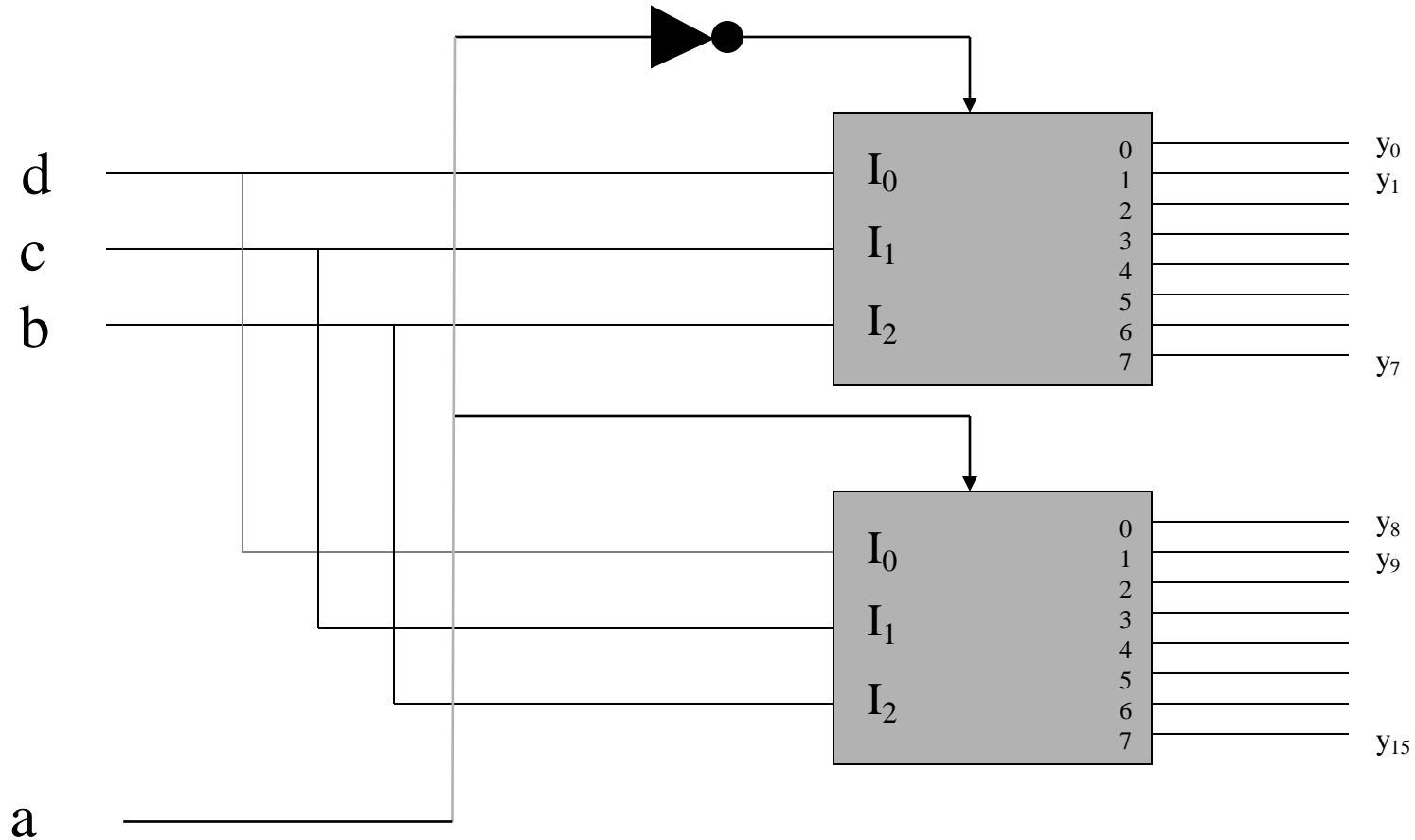Implement a $4\text{-}2^4$ decoder with $3\text{-}2^3$ decoders.



Tree of Decoders

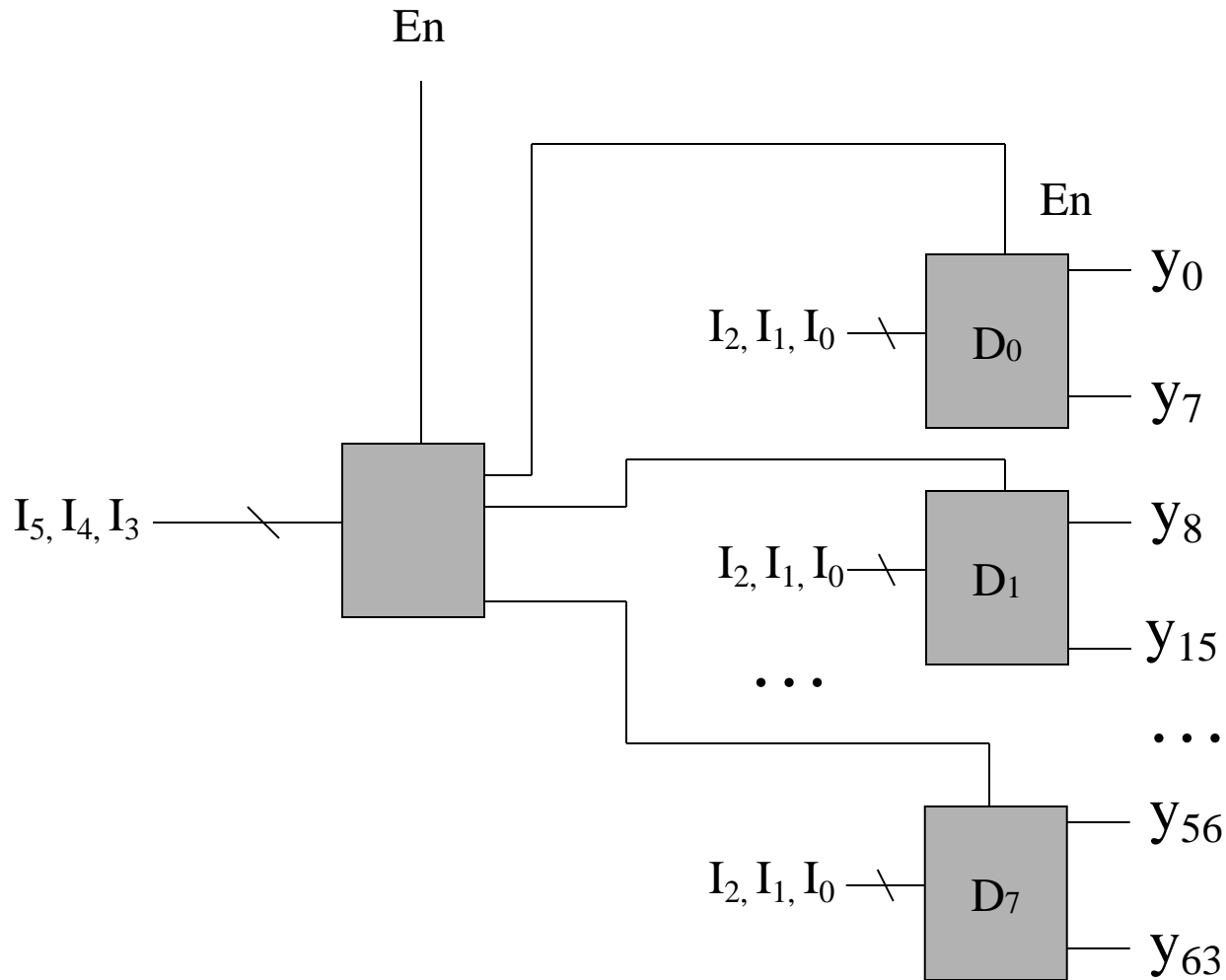
Implement a $6\text{-}2^6$ decoder with $3\text{-}2^3$ decoders.




2. Encoder

- Definition
- Logic Diagram
- Priority Encoder

2. Encoder: Definition

 

Encoder Description:

 

At most one $I_i = 1$.


$(y_{n-1}, \dots, y_0) = i$ if $I_i = 1$ & $En = 1$

$(y_{n-1}, \dots, y_0) = 0$ otherwise.


$A = 1$ if $En = 1$ and one i s.t. $I_i = 1$

$A = 0$ otherwise.

Encoder: Logic Diagram

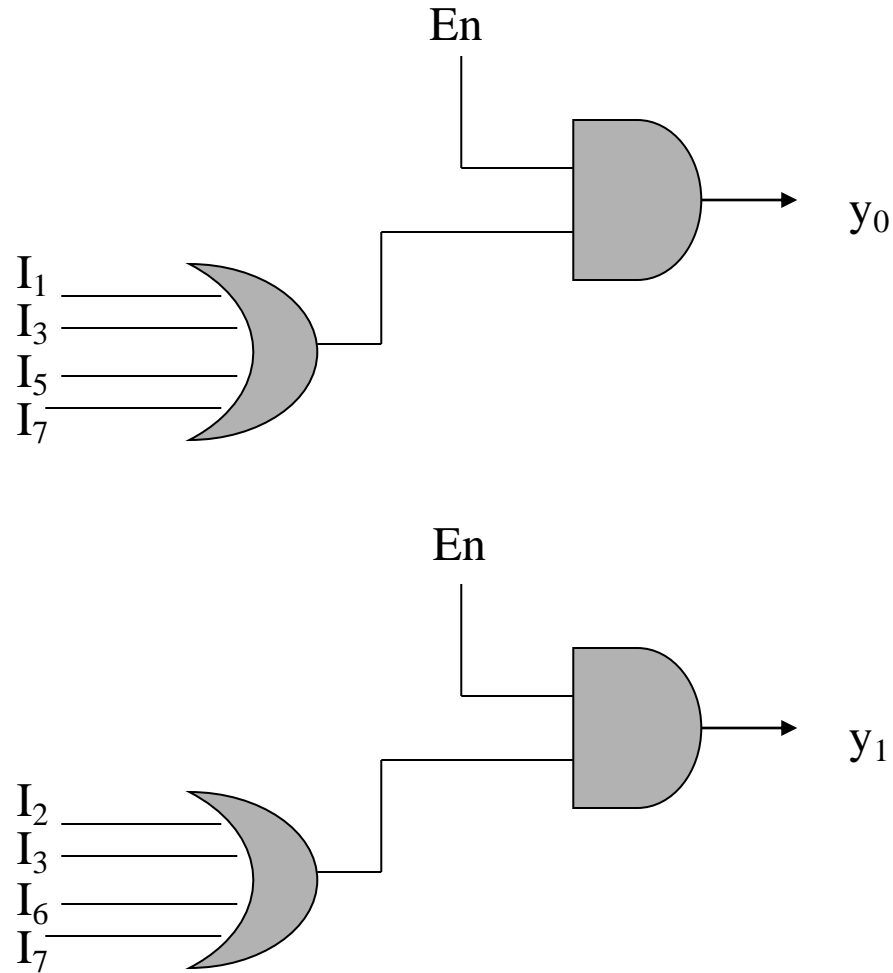


Encoder: Logic Diagram

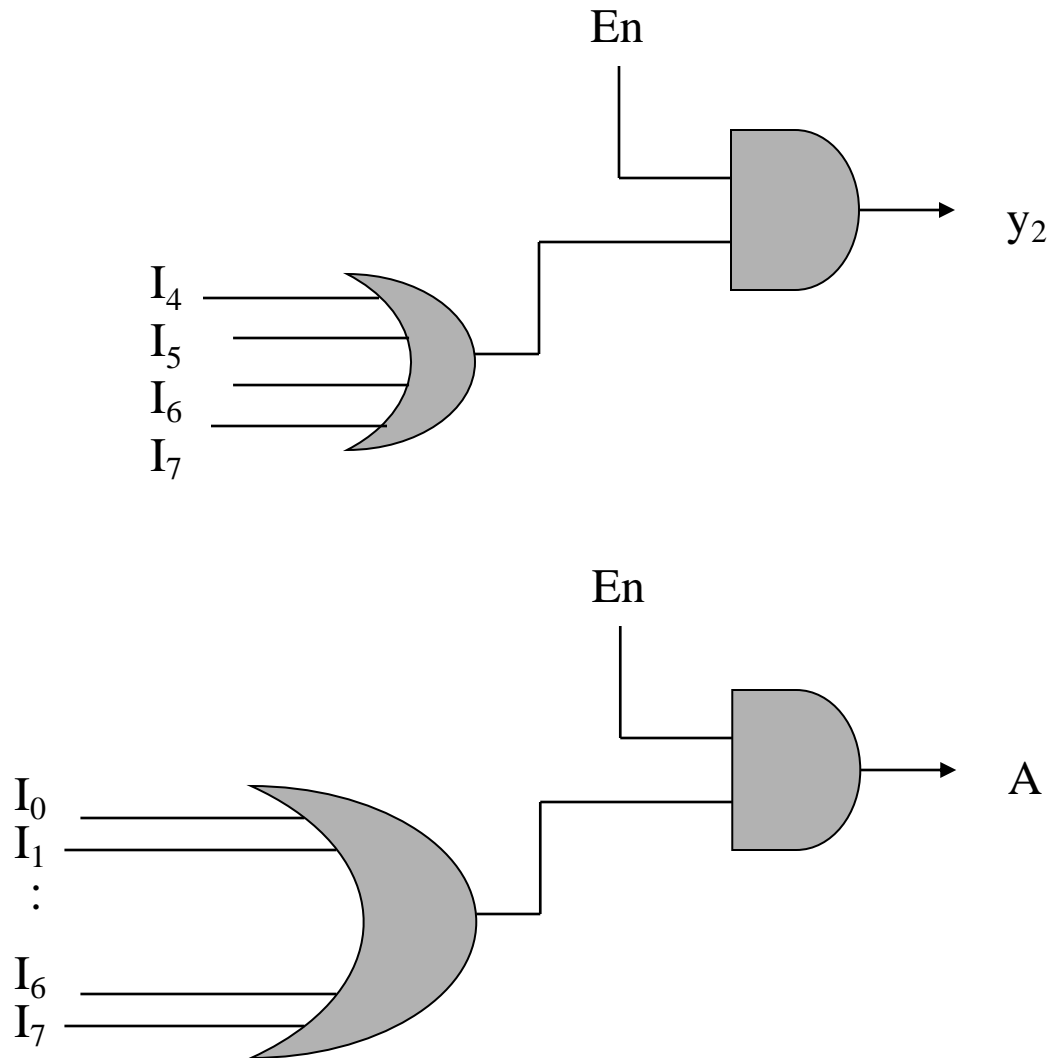

Priority Encoder: Definition

Description: Input (I_{2^n-1}, \dots, I_0), Output (y_{n-1}, \dots, y_0)

 $(y_{n-1}, \dots, y_0) = i$ if $I_i = 1$ & $En = 1$ & $I_k = 0$
for all $k > i$ (high bit priority) or
for all $k < i$ (low bit priority).




$E_o = 1$ if $En = 1$ & $I_i = 0$ for all i ,

$G_s = 1$ if $En = 1$ & $\exists i$ s.t. $I_i = 1$.

(G_s is like A , and E_o tells us if enable is true or not).

 
Priority Encoder: Implement a 32-input priority encoder w/ 8 input priority encoders (high bit priority).



Multiplexer

- Also called data selectors.
- Basic function: select one of its 2^n data input lines and place the corresponding information onto a single output line.
- n input bits needed to specify which input line is to be selected.
 - Place binary code for a desired data input line onto its n select input lines.



Realization of 4-to-1 line

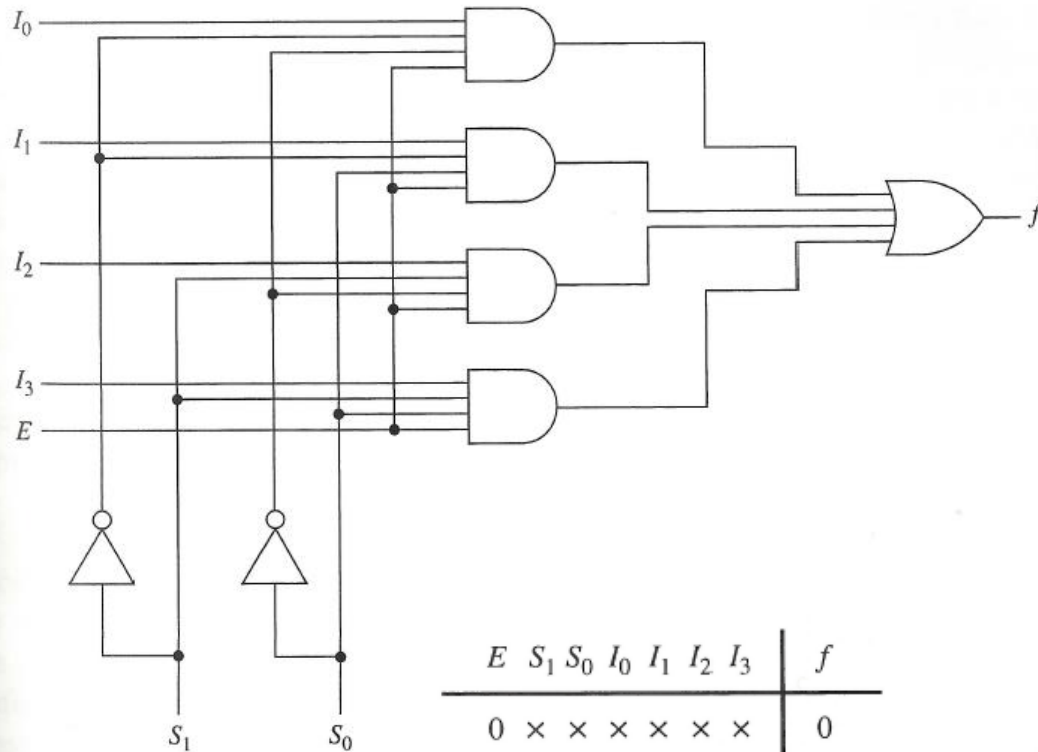

Logic Diagram

| E | S_1 | S_0 | I_0 | I_1 | I_2 | I_3 | f |
|-----|-------|-------|-------|-------|-------|-------|-----|
| 0 | x | x | x | x | x | x | 0 |
| 1 | 0 | 0 | 0 | x | x | x | 0 |
| 1 | 0 | 0 | 1 | x | x | x | 1 |
| 1 | 0 | 1 | x | 0 | x | x | 0 |
| 1 | 0 | 1 | x | 1 | x | x | 1 |
| 1 | 1 | 0 | x | x | 0 | x | 0 |
| 1 | 1 | 0 | x | x | 1 | x | 1 |
| 1 | 1 | 1 | x | x | x | 0 | 0 |
| 1 | 1 | 1 | x | x | x | 1 | 1 |

Truth Table

  

Symbol

Realization of 4-to-1 line multiplexer

- Alternate description:


Table 5.6 Function table for a 4-to-1-line multiplexer

| E | S_1 | S_0 | f |
|-----|-------|-------|-------|
| 0 | × | × | 0 |
| 1 | 0 | 0 | I_0 |
| 1 | 0 | 1 | I_1 |
| 1 | 1 | 0 | I_2 |
| 1 | 1 | 1 | I_3 |

- Algebraic description of multiplexer:

$$f = (I_0 \bar{S}_1 \bar{S}_0 + I_1 \bar{S}_1 S_0 + I_2 S_1 \bar{S}_0 + I_3 S_1 S_0)E$$

Building a Large Multiplexer

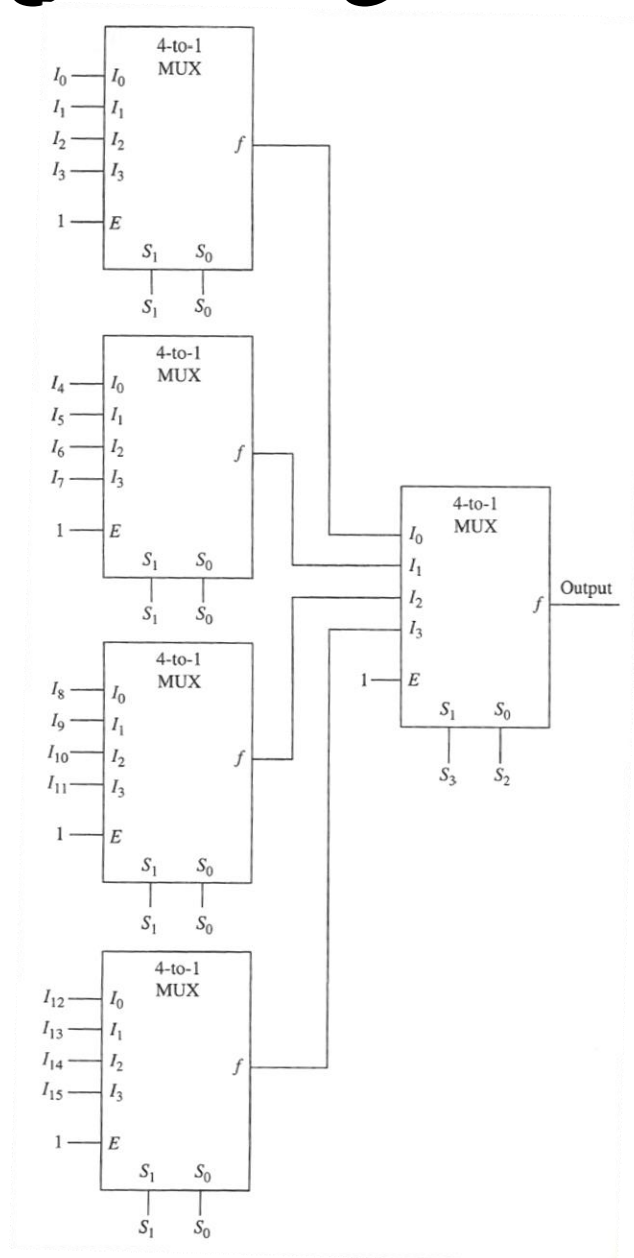

Multiplexers

- One of the primary applications of multiplexers is to provide for the transmission of information from several sources over a single path.
- This process is known as multiplexing.
- Demultiplexer = decoder with an enable input.

Multiplexer/De-multiplexer for information transmission

 


Figure 5.35 A multiplexer/demultiplexer arrangement for information transmission.