

Overview of CMOS & Logic Gates


- ❑ Introduction to CMOS circuits
- ❑ MOS transistor theory, processing technology
- ❑ CMOS circuit and logic design

Transistor Types

- ❑ Metal Oxide Semiconductor Field Effect Transistors
 - nMOS and pMOS MOSFETS
 - Voltage applied to insulated gate controls current between source and drain
 - Low power allows very high integration
- ❑ *Complementary Metal Oxide Semiconductor*
 - Fast, cheap, low power transistors


nMOS Transistor

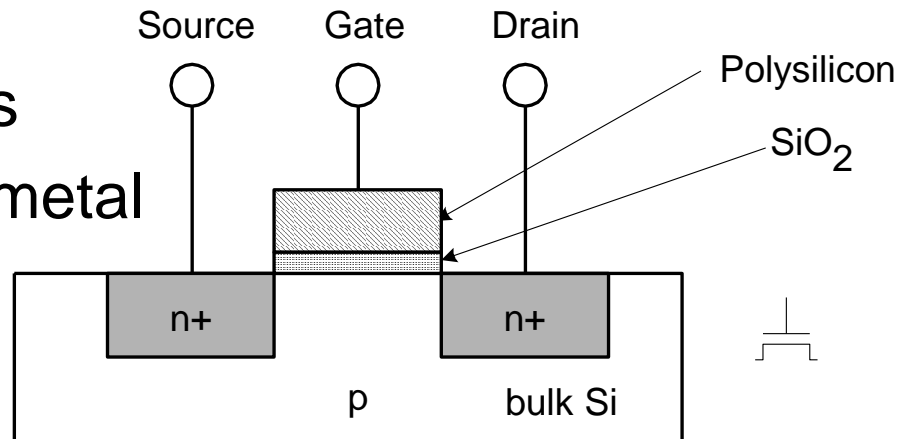- ❑ Four terminals: gate, source, drain, body
- ❑ Gate – oxide – body stack looks like a capacitor
 - Gate and body are conductors
 - SiO_2 (oxide) is a very good insulator
 - Called metal – oxide – semiconductor (MOS) capacitor
 - Even though gate is no longer made of metal




nMOS Operation

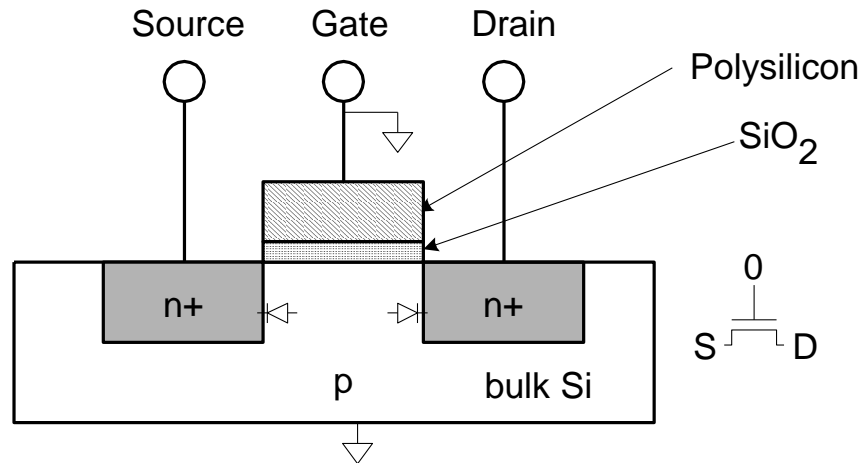- ❑ Body is commonly tied to ground (0 V)
- ❑ When the gate is at a low voltage:
 - P-type body is at low voltage
 - Source-body and drain-body diodes are OFF
 - No current flows, transistor is OFF




nMOS Operation Cont.

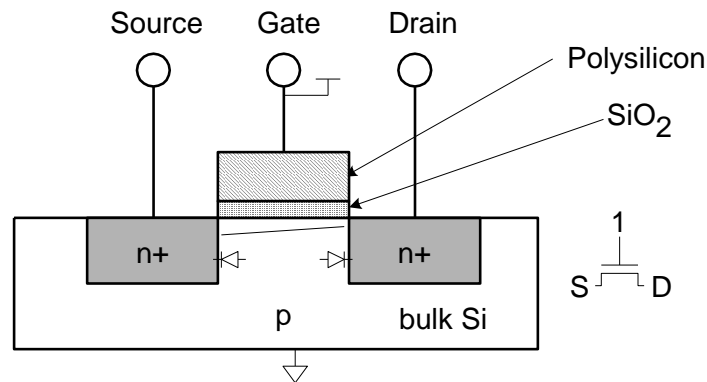- When the gate is at a high voltage:
 - Positive charge on gate of MOS capacitor
 - Negative charge attracted to body
 - Inverts a channel under gate to n-type
 - Now current can flow through n-type silicon from source through channel to drain, transistor is ON



pMOS Transistor

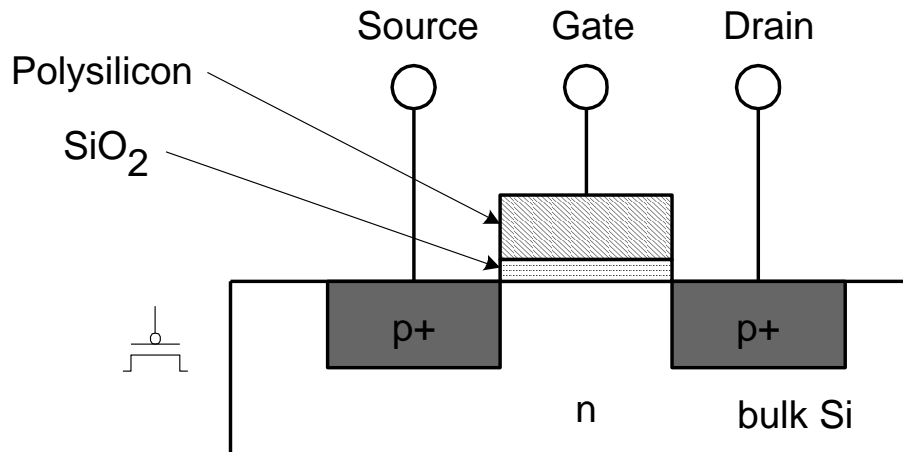- ❑ Similar, but doping and voltages reversed
 - Body tied to high voltage (V_{DD})
 - Gate low: transistor ON
 - Gate high: transistor OFF
 - Bubble indicates inverted behavior




Power Supply Voltage

- ❑ $GND = 0\text{ V}$
- ❑ In 1980's, $V_{DD} = 5\text{V}$
- ❑ V_{DD} has decreased in modern processes
 - High V_{DD} would damage modern tiny transistors
 - Lower V_{DD} saves power
- ❑ $V_{DD} = 3.3, 2.5, 1.8, 1.5, 1.2, 1.0, \dots$



Transistors as Switches

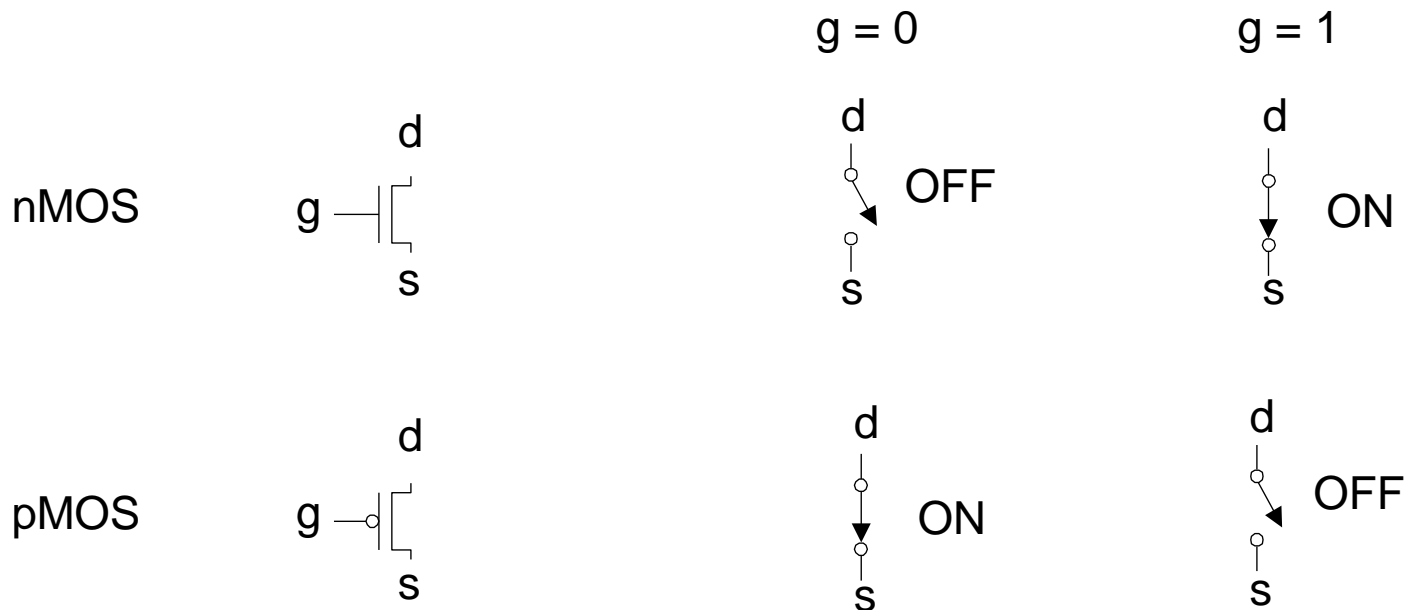- ❑ We can view MOS transistors as electrically controlled switches
- ❑ Voltage at gate controls path from source to drain





CMOS Inverter

A	Y
0	
1	

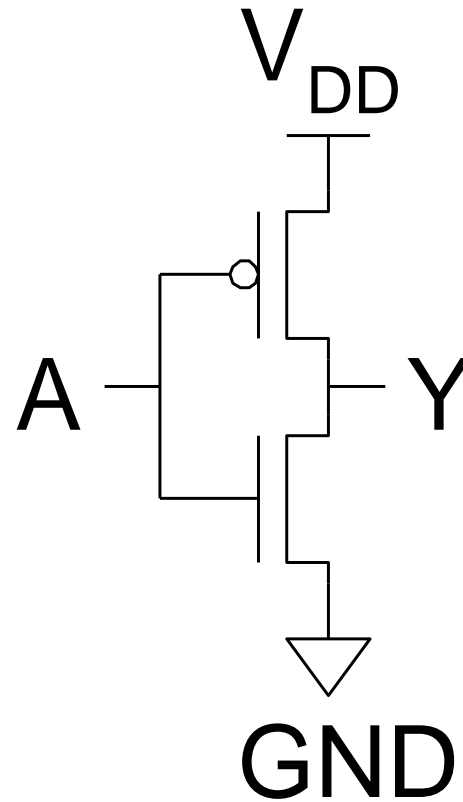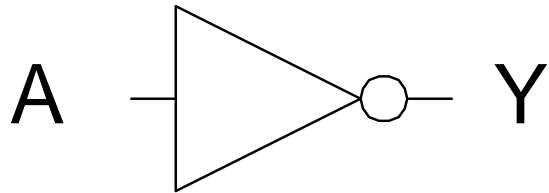



CMOS Inverter

A	Y
0	
1	0

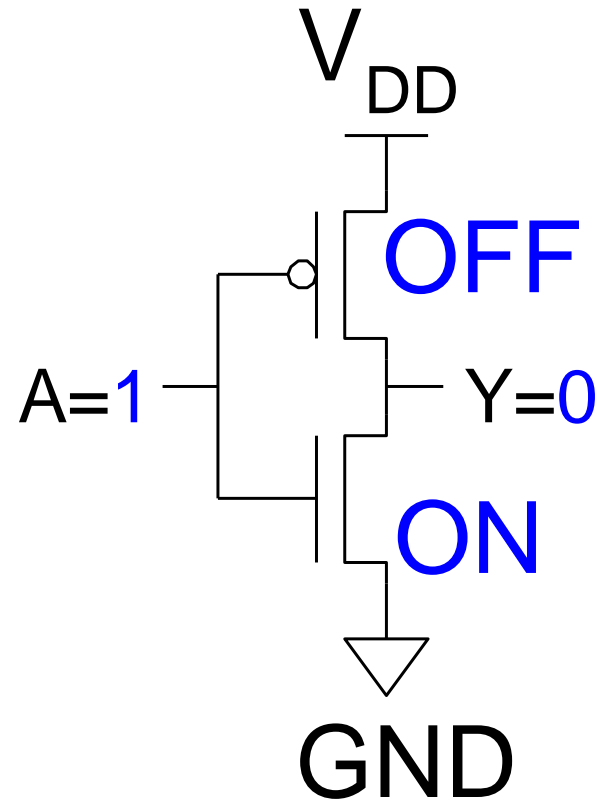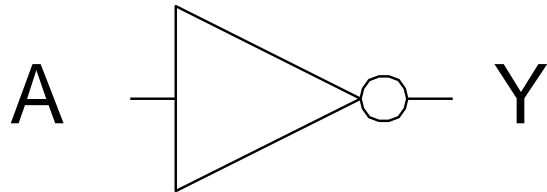



CMOS Inverter

A	Y
0	1
1	0

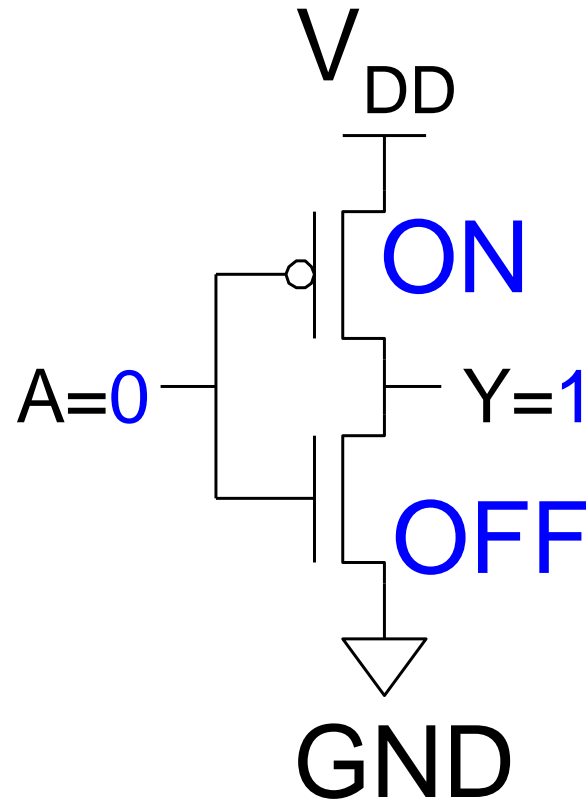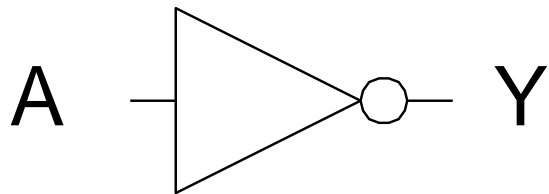



CMOS NAND Gate

A	B	Y
0	0	
0	1	
1	0	
1	1	

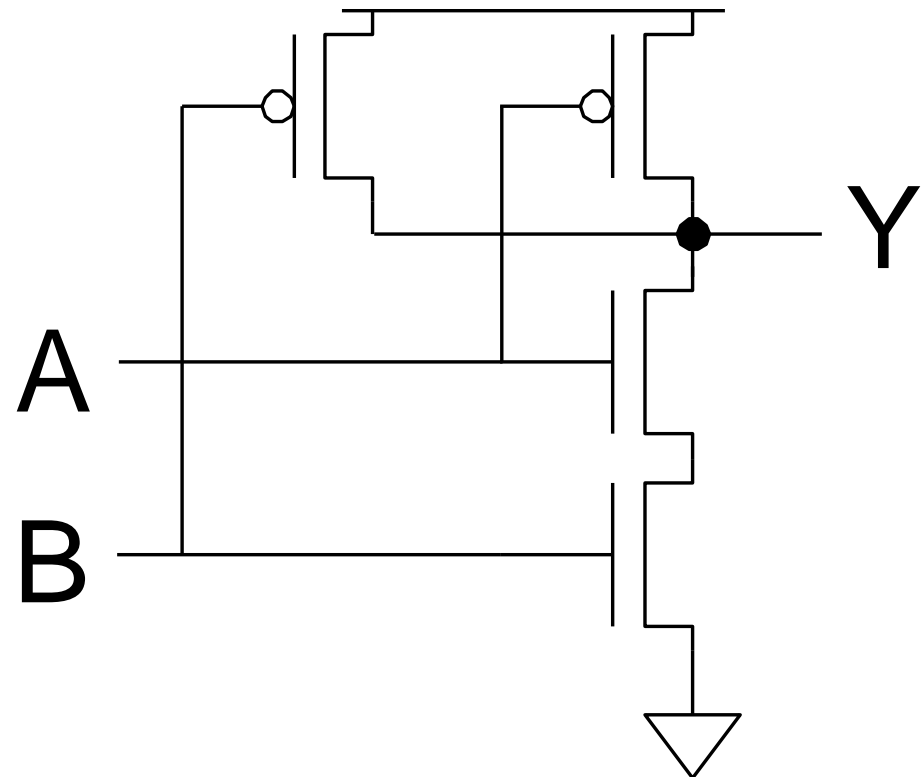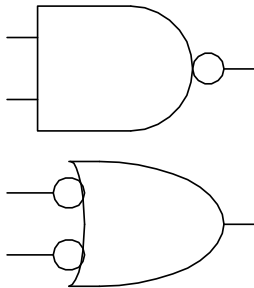



CMOS NAND Gate

A	B	Y
0	0	1
0	1	
1	0	
1	1	

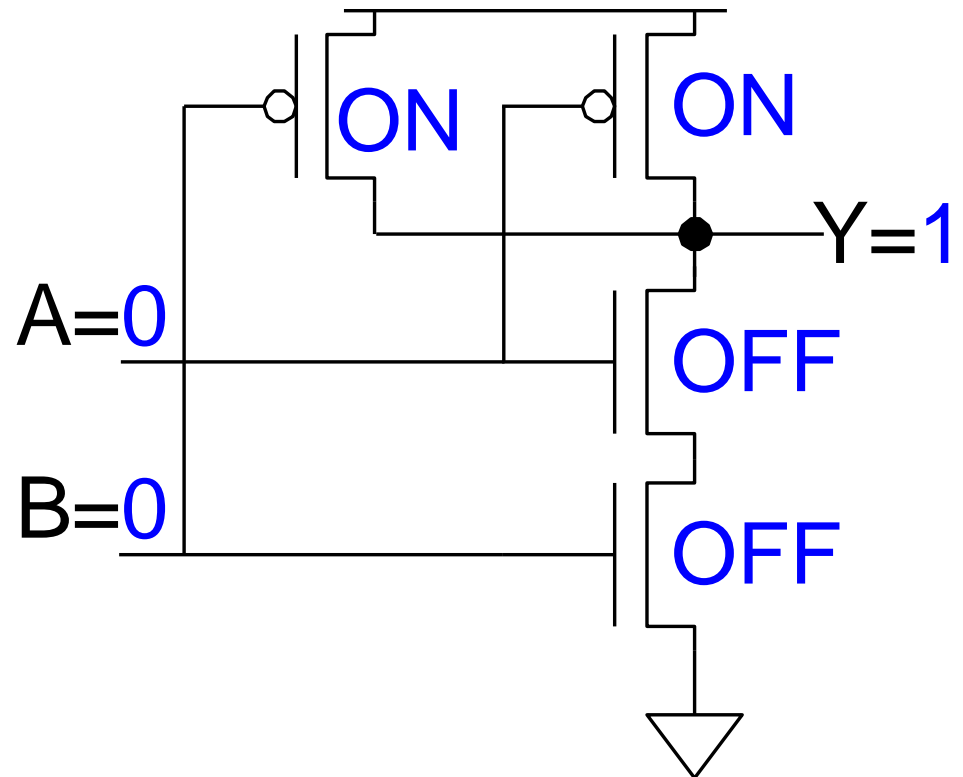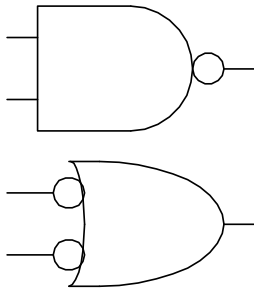



CMOS NAND Gate

A	B	Y
0	0	1
0	1	1
1	0	
1	1	

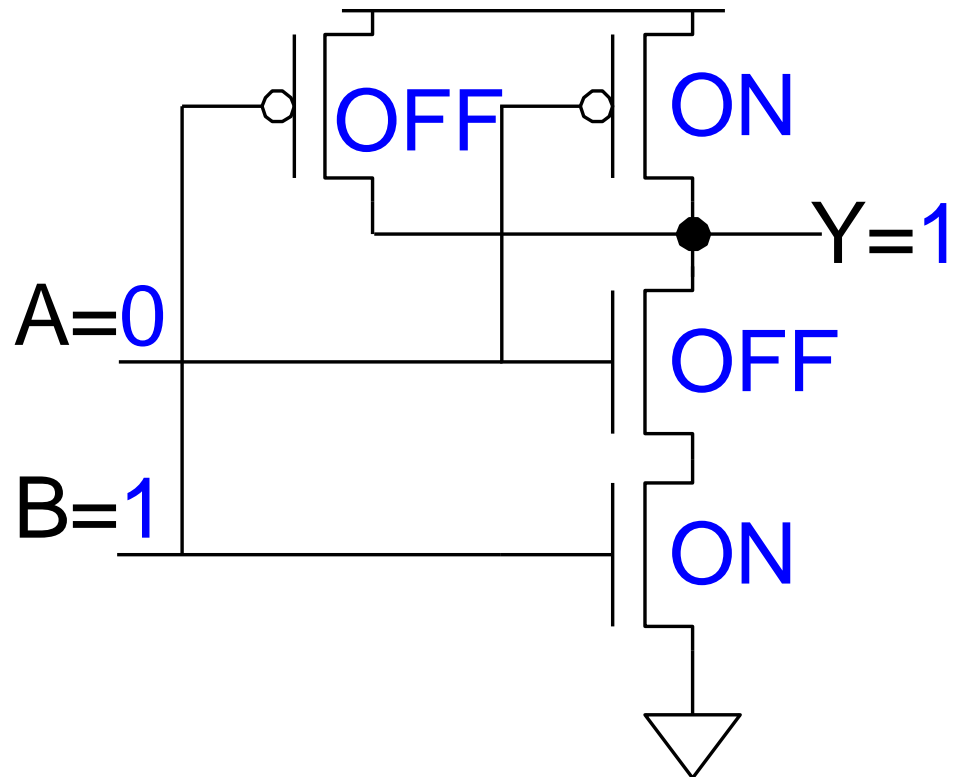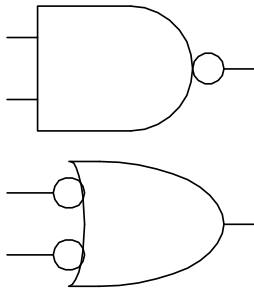



CMOS NAND Gate

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	

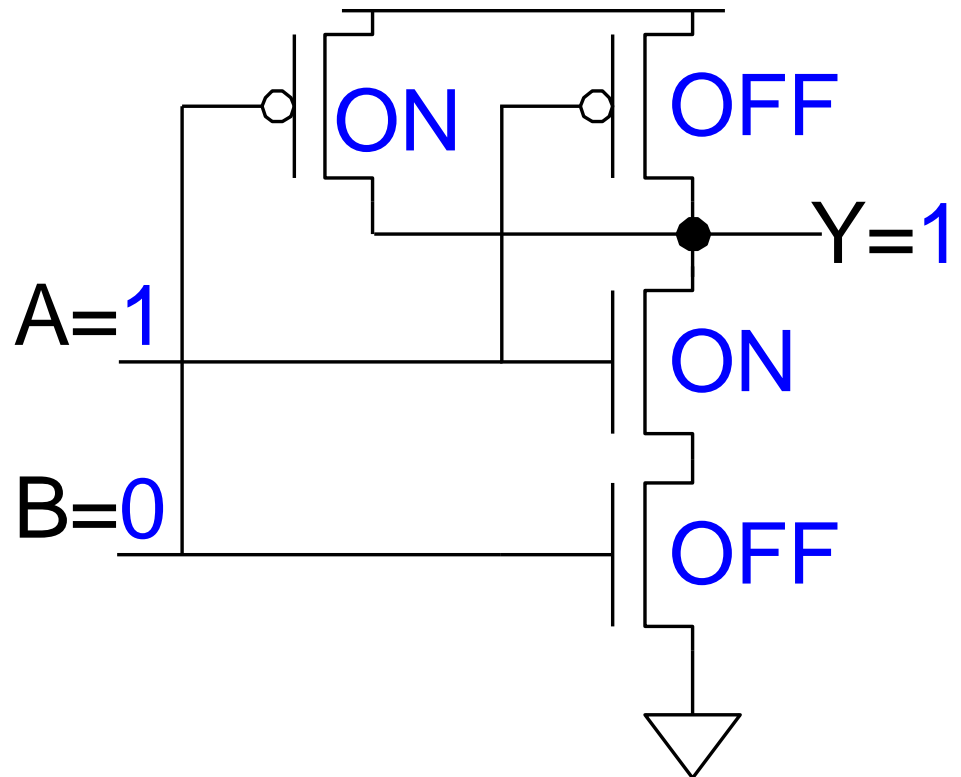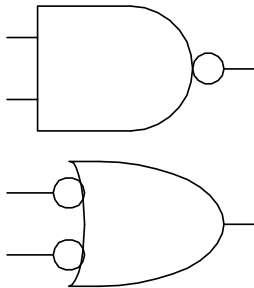



CMOS NAND Gate

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

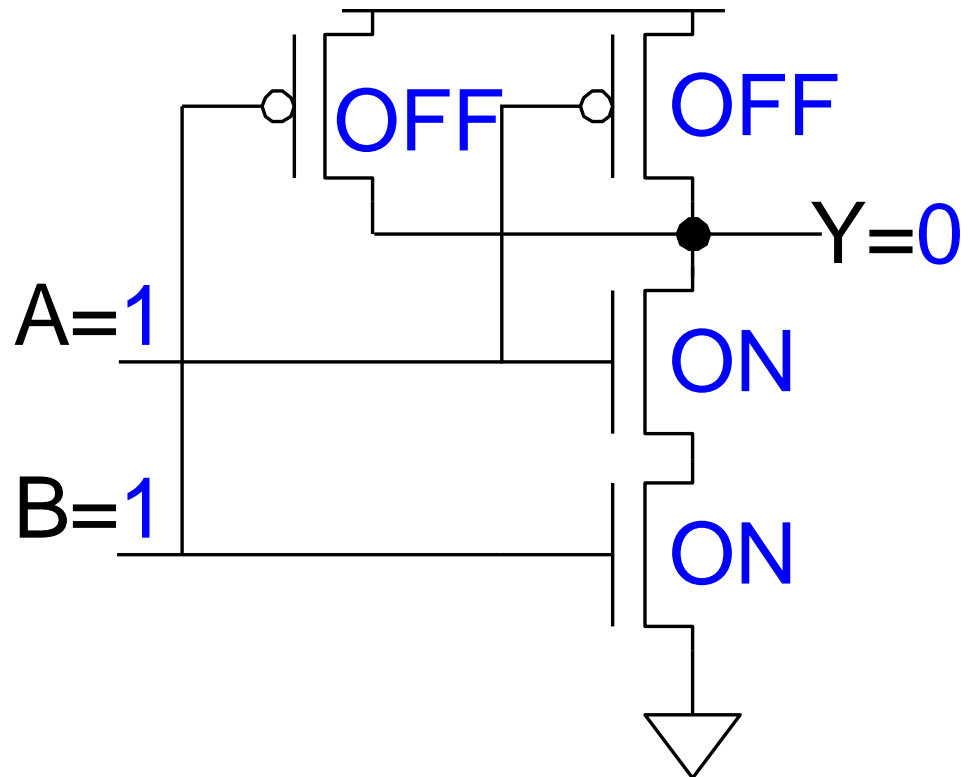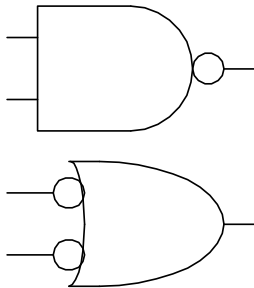


CMOS NOR Gate

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

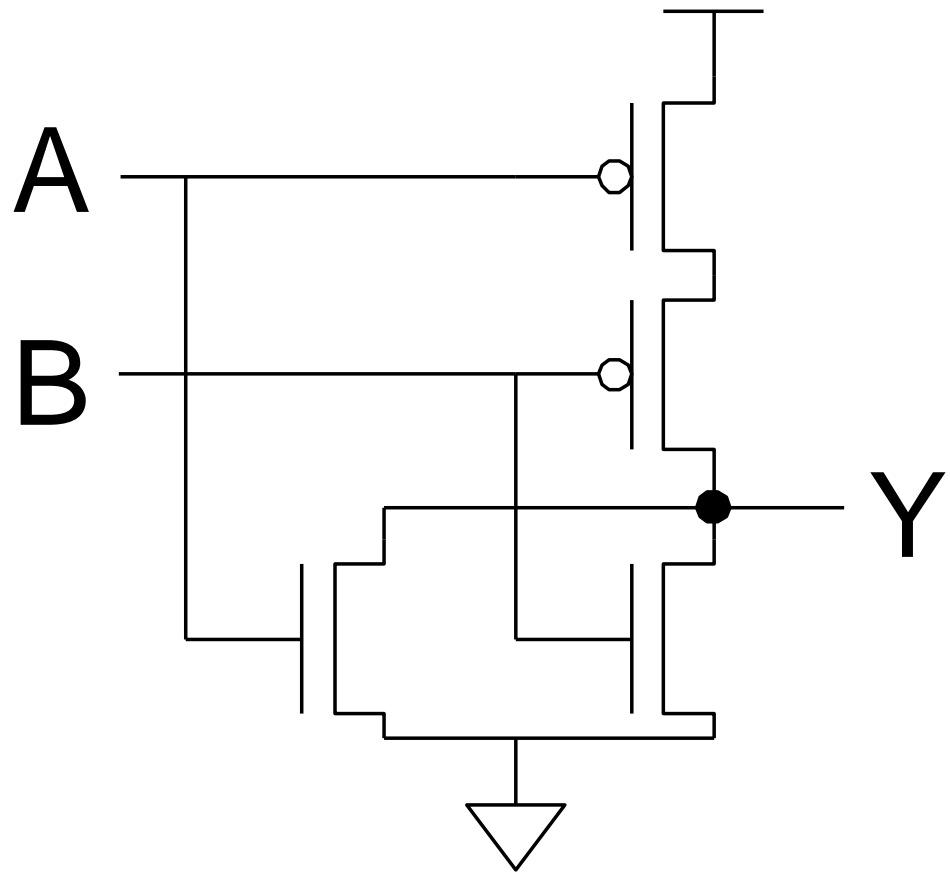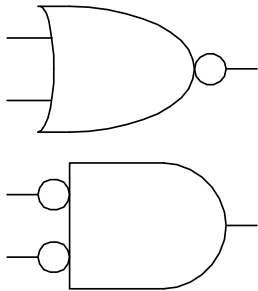


3-input NAND Gate

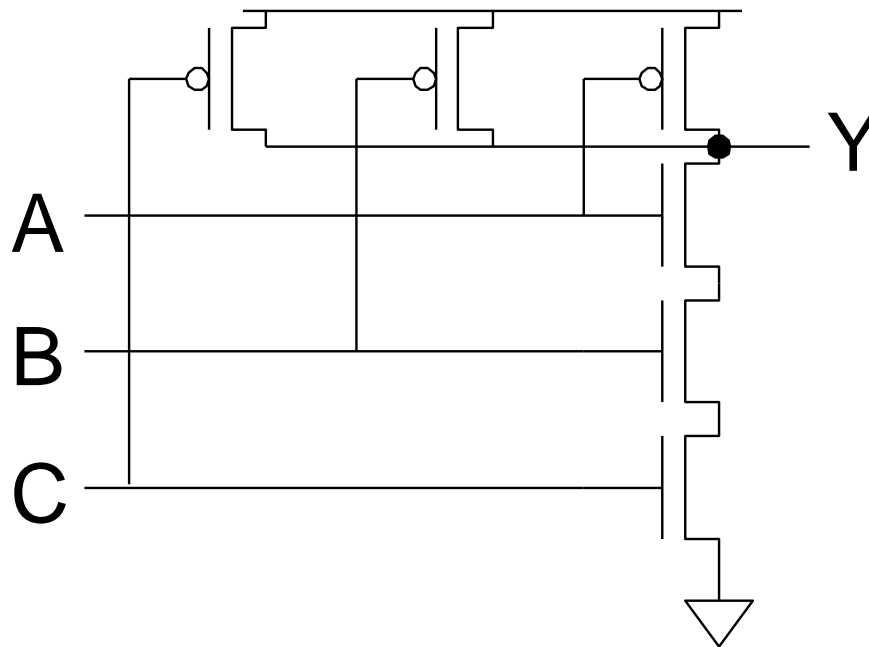- ❑ Y pulls low if ALL inputs are 1
- ❑ Y pulls high if ANY input is 0



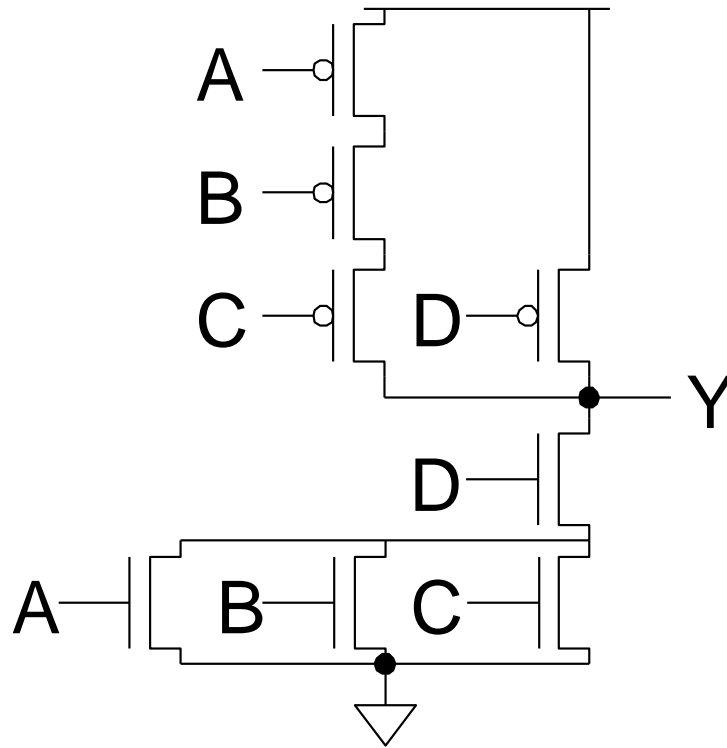Example: O3AI

$$\square Y = \overline{(A + B + C)} \square D$$



CMOS Fabrication

- ❑ CMOS transistors are fabricated on silicon wafer
- ❑ Lithography process similar to printing press
- ❑ On each step, different materials are deposited or etched
- ❑ Easiest to understand by viewing both top and cross-section of wafer in a simplified manufacturing process

Well and Substrate Taps

- ❑ Substrate must be tied to GND and n-well to V_{DD}
- ❑ Metal to lightly-doped semiconductor forms poor connection (used for Schottky Diode)
- ❑ Use heavily doped well and substrate contacts / taps

