

# Computer Architecture (Processor Design - Hardware)



विद्याधनं सर्वधनं प्रधानम्

**Subhasis Bhattacharjee**

Department of Computer Science and Engineering,  
Indian Institute of Technology, Jammu

June 27, 2023

# Outline

- 1 Instruction Fetch Unit
- 2 Instruction Set & Format
- 3 Register File

# Processor Design

## The aim of processor design

- Implement the entire SimpleRisc ISA
- Process the binary format of instructions
- Provide as much of performance as possible

## Basic Approach

- Divide the processing into stages
- Design each stage separately

# Data Path and Control Path


## Data Path

The data path consists of all the elements in a processor that are dedicated to storing, retrieving, and processing data such as register files, memory, and the ALU.

## Control Path


The control path primarily contains the control unit, whose role is to generate the appropriate signals to control the movement of instructions, and data in the data path.

# Control Path

 

[ We will look at the hardwired control path ]

# A Processor Divided Into Stages

 

# Instruction Fetch (IF)

## Instruction Fetch (IF)

- Fetch an instruction from the instruction memory
- Compute the address of the next instruction

# Operand Fetch (OF) Stage

## Operand Fetch (OF)

- Decode the instruction (break it into fields)
- Fetch the register operands from the register file
- Compute the branch target ( $PC + \text{offset}$ )
- Compute the immediate (16 bits + 2 modifiers)
- Generate control signals (we will see later)



# Execute (EX) Stage

## Execute (EX)

- The EX Stage
- Contains an Arithmetic-Logical Unit (ALU)
- This unit can perform all arithmetic operations ( add, sub, mul, div, cmp, mod), and logical operations (and, or, not)
- Contains the branch unit for computing the branch condition (beq, bgt)
- Contains the flags register (updated by the cmp instruction)

# MA and RW Stages

## MA (Memory Access) Stage


- Interfaces with the memory system
- Executes a load or a store

## RW (Register Write) Stage

- Writes to the register file
- In the case of a call instruction, it writes the return address to register, ra

## Instruction Fetch Unit

# Instruction Fetch (IF) Stage

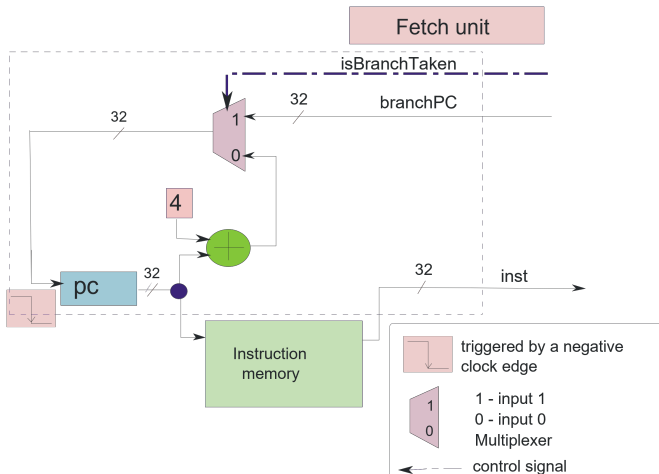

[ negative edge triggered - assumed ]

# The Fetch unit

- The pc register contains the program counter
- We use the pc to access the instruction memory
- The multiplexer chooses between
  - ①  $pc + 4$
  - ② branchTarget
- It uses a control signal  $\rightarrow$  isBranchTaken

# isBranchTaken - Signal

- isBranchTaken is a control signal
- It is generated by the EX unit (We will see it in the EX unit)

## Conditions on isBranchTaken

Instruction	Value of isBranchTaken
non-branch instruction	0
call	1
ret	1
b	1
beq	branch taken = 1
	branch not taken = 0
bgt	branch taken = 1
	branch not taken = 0

# Data Path and Control Path - revisiting


## Data Path

The data path consists of all the elements in a processor that are dedicated to storing, retrieving, and processing data such as register files, memory, and the ALU.

## Control Path

The control path primarily contains the control unit, whose role is to generate the appropriate signals to control the movement of instructions, and data in the data path.

# Control Path

 



# Instruction Set & Format

# Instruction Set - at a glance

Inst.	Code	Format	Inst.	Code	Format
add	00000	add rd, rs1, (rs2/imm)	lsl	01010	lsl rd, rs1, (rs2/imm)
sub	00001	sub rd, rs1, (rs2/imm)	lsr	01011	lsr rd, rs1, (rs2/imm)
mul	00010	mul rd, rs1, (rs2/imm)	asr	01100	asr rd, rs1, (rs2/imm)
div	00011	div rd, rs1, (rs2/imm)	nop	01101	nop
mod	00100	mod rd, rs1, (rs2/imm)	ld	01110	ld rd, imm[rs1]
cmp	00101	cmp rs1, (rs2/imm)	st	01111	st rd, imm[rs1]
and	00110	and rd, rs1, (rs2/imm)	beq	10000	beq offset
or	00111	or rd, rs1, (rs2/imm)	bgt	10001	bgt offset
not	01000	not rd, (rs2/imm)	b	10010	b offset
mov	01001	mov rd, (rs2/imm)	call	10011	call offset
			ret	10100	ret


# Instruction Formats

Format	Definition					
<i>branch</i>	<i>op</i> (28-32)	<i>offset</i> (1-27)				
<i>register</i>	<i>op</i> (28-32)	<i>I</i> (27)	<i>rd</i> (23-26)	<i>rs1</i> (19-22)	<i>rs2</i> (15-18)	
<i>immediate</i>	<i>op</i> (28-32)	<i>I</i> (27)	<i>rd</i> (23-26)	<i>rs1</i> (19-22)	<i>imm</i> (1-18)	
<i>op</i> → opcode, <i>offset</i> → branch offset, <i>I</i> → immediate bit, <i>rd</i> → destination register						
<i>rs1</i> → source register 1, <i>rs2</i> → source register 2, <i>imm</i> → immediate operand						

[ Each format needs to be handled separately. ]

# Register File

# Register File Read

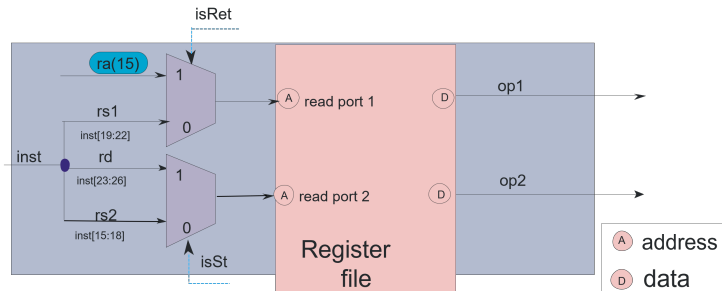

## Two Input Lines

- First input → *rs1* or *ra(15)* (ret instruction)
- Second input → *rs2* or *rd* (store instruction)

# Register File Access - Input / Output


The register file has two read ports

- 1st Input
- 2nd Input

The register file has two outputs (op1, and op2)


- op1 is the branch target (return address) in the case of a ret instruction, or rs1
- op2 is the value that needs to be stored in the case of a store instruction, or rs2

# Immediate and Branch Unit

 


- Compute immx (extended immediate), branchTarget, irrespective of the instruction format.
- For the branchTarget we need to choose between the embedded target and op1 (ret)

# OF Unit

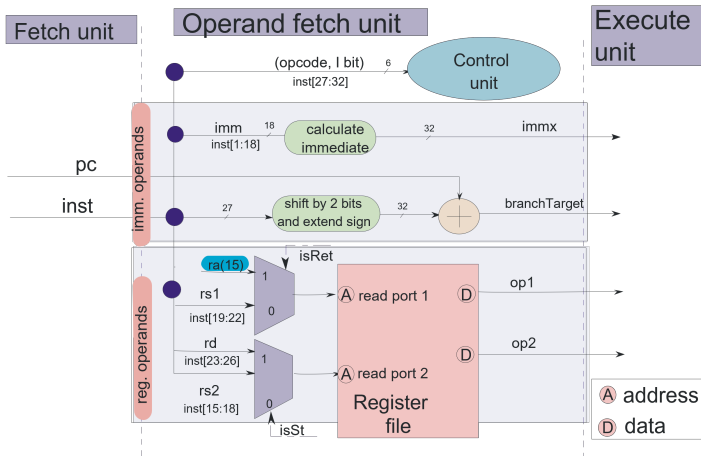




# EX Stage – Branch Unit

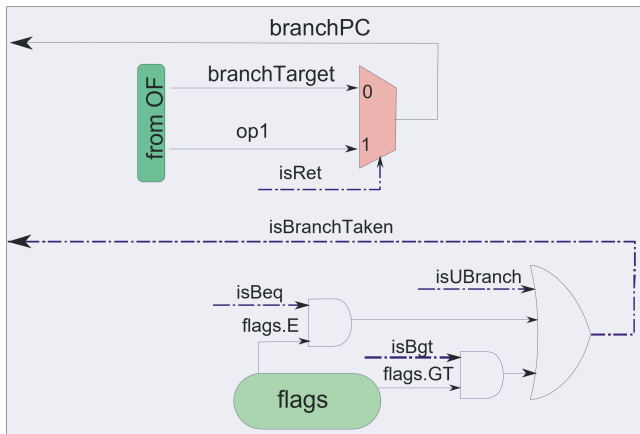


[ Generates the **isBranchTaken** Signal ]

# ALU

 


[ Choose between immx and op2 based on the value of the I bit ]


# Inside the ALU

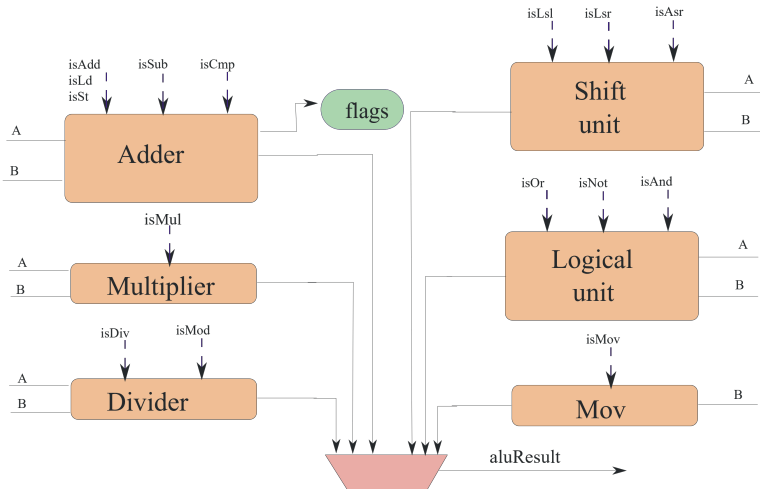


# EX Unit

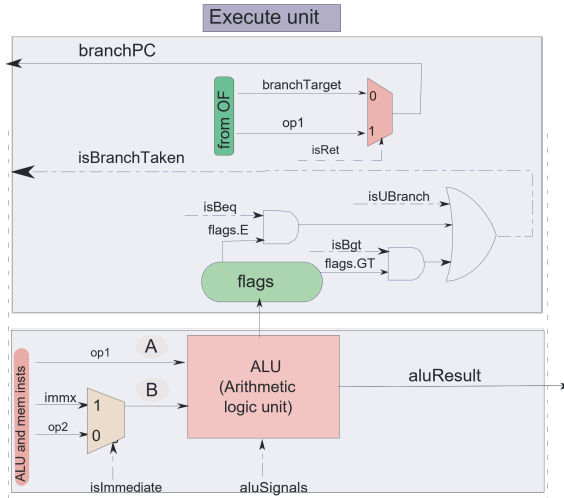


# MA Unit

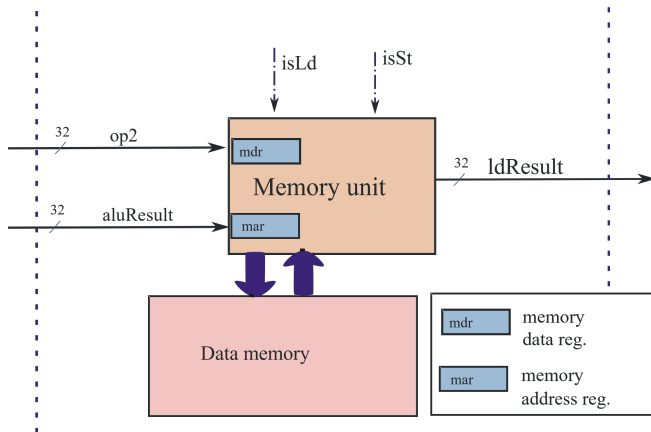

## RW Unit

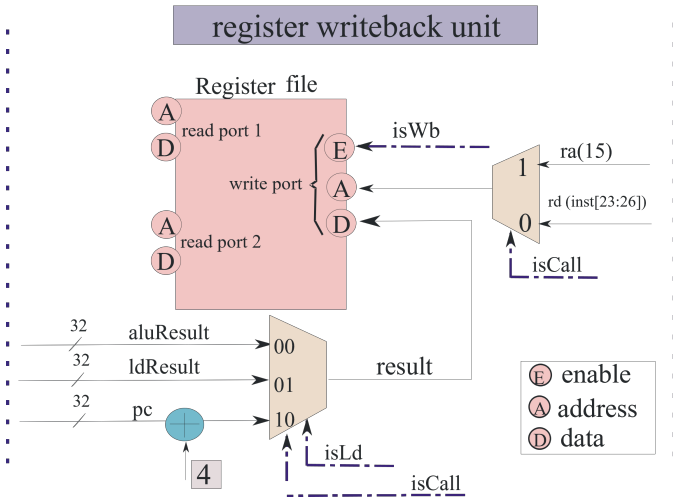
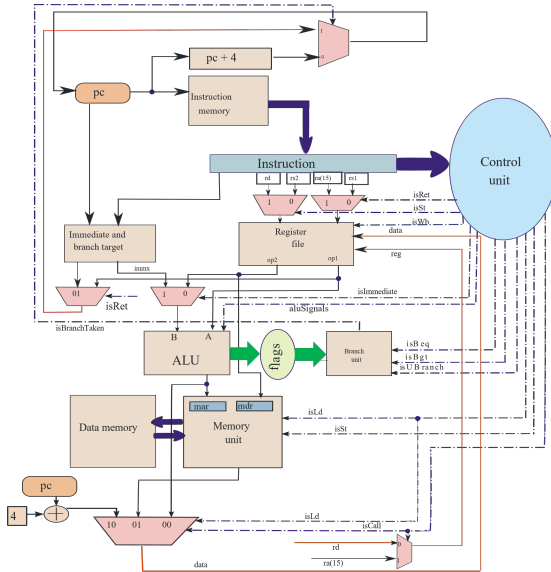
## Internal Details Of Five Stage Processor



# The Hardwired Control Unit



Given the opcode and the immediate (I) bit

It generates all the control signals.




# Control Signals

Sr. No.	Signal	Meaning / Explanation
1	isSt	Instruction: st
2	isLd	Instruction: ld
3	isBeq	Instruction: beq
4	isBgt	Instruction: bgt
5	isRet	Instruction: ret
6	isImmediate	I bit set to 1
7	isWb	Instructions: add, sub, mul, div, mod, and, or, not, mov, ld, lsl, lsr, asr, call
8	isUBranch	Instructions: b, call, ret
9	isCall	Instructions: call

# Control Signals – II

aluSignal		
Sr. No.	Signal	Meaning / Explanation
10	isAdd	Instructions: add, ld, st
11	isSub	Instruction: sub
12	isCmp	Instruction: cmp
13	isMul	Instruction: mul
14	isDiv	Instruction: div
15	isMod	Instruction: mod
16	isLsl	Instruction: lsl
17	isLsr	Instruction: lsr
18	isAsr	Instruction: asr
19	isOr	Instruction: or
20	isAnd	Instruction: and
21	isNot	Instruction: not
22	isMov	Instruction: mov
 
# Bits of Instructions to Generate These Signals



opcode



immediate bit

# Control Signals

Sr. No.	Signal	Condition / Boolean Logic
1	isSt	$\overline{\text{op5}}.\overline{\text{op4}}.\overline{\text{op3}}.\overline{\text{op2}}.\overline{\text{op1}}$
2	isLd	$\overline{\text{op5}}.\overline{\text{op4}}.\overline{\text{op3}}.\overline{\text{op2}}.\overline{\text{op1}}$
3	isBeq	$\text{op5}.\overline{\text{op4}}.\overline{\text{op3}}.\overline{\text{op2}}.\overline{\text{op1}}$
4	isBgt	$\text{op5}.\overline{\text{op4}}.\overline{\text{op3}}.\overline{\text{op2}}.\overline{\text{op1}}$
5	isRet	$\text{op5}.\overline{\text{op4}}.\overline{\text{op3}}.\overline{\text{op2}}.\overline{\text{op1}}$
6	isImmediate	1
7	isWb	$\neg(\text{op5} + \overline{\text{op5}}.\overline{\text{op3}}.\overline{\text{op1}}.(\text{op4} + \text{op2})) + \text{op5}.\overline{\text{op4}}.\overline{\text{op3}}.\overline{\text{op2}}.\overline{\text{op1}}$
8	isUBranch	$\text{op5}.\overline{\text{op4}}.(\overline{\text{op3}}.\overline{\text{op2}} + \text{op3}.\overline{\text{op2}}.\overline{\text{op1}})$
9	isCall	$\text{op5}.\overline{\text{op4}}.\overline{\text{op3}}.\overline{\text{op2}}.\overline{\text{op1}}$

# Control Signals – II

aluSignal		
Sr. No.	Signal	Meaning / Explanation
10	isAdd	$\overline{\text{op5}}.\overline{\text{op4}}.\overline{\text{op3}}.\overline{\text{op2}}.\overline{\text{op1}} + \overline{\text{op5}}.\overline{\text{op4}}.\overline{\text{op3}}.\overline{\text{op2}}$
11	isSub	$\overline{\text{op5}}.\overline{\text{op4}}.\overline{\text{op3}}.\overline{\text{op2}}.\overline{\text{op1}}$
12	isCmp	$\overline{\text{op5}}.\overline{\text{op4}}.\overline{\text{op3}}.\overline{\text{op2}}.\overline{\text{op1}}$
13	isMul	$\overline{\text{op5}}.\overline{\text{op4}}.\overline{\text{op3}}.\overline{\text{op2}}.\overline{\text{op1}}$
14	isDiv	$\overline{\text{op5}}.\overline{\text{op4}}.\overline{\text{op3}}.\overline{\text{op2}}.\overline{\text{op1}}$
15	isMod	$\overline{\text{op5}}.\overline{\text{op4}}.\overline{\text{op3}}.\overline{\text{op2}}.\overline{\text{op1}}$
16	isLsl	$\overline{\text{op5}}.\overline{\text{op4}}.\overline{\text{op3}}.\overline{\text{op2}}.\overline{\text{op1}}$
17	isLsr	$\overline{\text{op5}}.\overline{\text{op4}}.\overline{\text{op3}}.\overline{\text{op2}}.\overline{\text{op1}}$
18	isAsr	$\overline{\text{op5}}.\overline{\text{op4}}.\overline{\text{op3}}.\overline{\text{op2}}.\overline{\text{op1}}$
19	isOr	$\overline{\text{op5}}.\overline{\text{op4}}.\overline{\text{op3}}.\overline{\text{op2}}.\overline{\text{op1}}$
20	isAnd	$\overline{\text{op5}}.\overline{\text{op4}}.\overline{\text{op3}}.\overline{\text{op2}}.\overline{\text{op1}}$
21	isNot	$\overline{\text{op5}}.\overline{\text{op4}}.\overline{\text{op3}}.\overline{\text{op2}}.\overline{\text{op1}}$
22	isMov	$\overline{\text{op5}}.\overline{\text{op4}}.\overline{\text{op3}}.\overline{\text{op2}}.\overline{\text{op1}}$